

Devre Teorisi:

- 23 Mart 1. Kısa Süreç
- 25 Mayıs 2. Kısa Süreç

homza Osman İlhan
hoilhan@yildiz.edu.tr

units of measurement - Basic Terminologies in Circuits - ~~part 1~~
 circuit components - Ohm's law

 units of measurement :

• Length	meter	m	10^9	giga	G
• Mass	kilogram	kg	10^6	Mega	M
• Time	second	s	10^3	kilo	K
• Electric current	ampere	A		-	
• Thermodynamic temperature	Kelvin	K	10^{-3}	milli	m
• Luminous intensity	Candela	cd	10^{-6}	micro	μ
• charge	coulomb	C	10^{-9}	nano	n
			10^{-12}	pico	p

* Scientific notations : tek decimal

$$\bullet \frac{1}{16} = 6.25 E-2 = 6.25 \times 10^{-2}$$


$$\bullet 1/3 = 3.33 E-1$$

* Engineering notation : 1, 2 veya 3 decimal atabil

$$\bullet \frac{1}{16} = 62.5 E-3$$

$$\bullet 1/3 = 333.33 E-3$$

Electricity

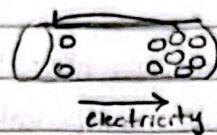

o = electron


→ Electricity is a result from the flow of electrons

→ Electricity flows in the opposite direction of electron flow

⊕ Electricity is similar to water flow:

- water flows from high level to low level

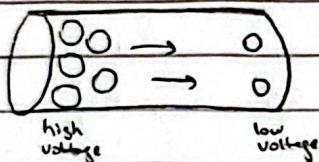- Electricity flows from high voltage to low voltage



⊕ akımın akması için
yük farklılığı olması lazımdır

⊕ Potansiyel fark arttıkça
akım hızı artar veya yoksa
akım olurdu

Circuit Components

- Active elements

- independent power sources

- voltage, current (akım)

- dependent power sources

- voltage, current

- Measurement Devices

- Ampermeters

- measure current

- Voltmeters

- measure voltage

- Passive Elements

- Resistors

- Capacitors

- inductors

- Ground

- Reference point

- Electric Wire (elektrik tel)


- Protective Devices

- Fuse (sigorta)

- Switches

independent power sources

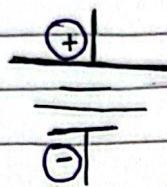1- independent voltage source outputs a voltage to the circuit no matter how much current is required



2- independent current source outputs a dc or ac current to the circuit no matter how much voltage is required




Example 1

the current source is generated

$$1V (3A) = 3W \quad (P = V \cdot I)$$

$$P = -3A(1V) = -3W$$

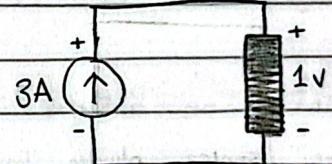

$$\sum P = P_{\text{current source}} + P_{\text{res element}} = 0$$

cirdeğ olmuy
tabii


* artıdon akım akırsa giderdir.
ortodon akım giderse tekrichtir.

Dependent Power Sources


- Voltage controlled voltage source (VCVS)



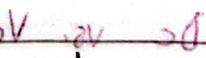- Current controlled voltage source (CCVS)



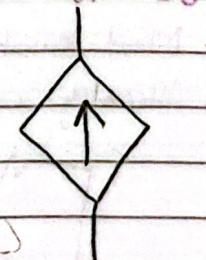- Voltage controlled current source (VCCS)



- Current controlled current source (CCCS)

DA

DC

Passive Elements

Resistor




ohm Ω

inductor



henry H

Capacitor

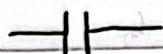

Farad F

Other basic circuit elements

Electric wire



Ground



Switch



Fuse (sigorta)



* All points on a same electric wire have the same voltage

* A voltage source always have volt difference of its pins equal to its value

* Ground always has zero voltage (0 volts)



current, the flow of charge through a cross-sectional area as a function of time or the time rate of change of charge. Symbol used is I or i

$$i = \frac{dq}{dt} \quad q = \text{charge} \quad t = \text{time} \quad i = \text{current}$$

Dc vs. Vc :

- Direct current \rightarrow current remains constant with time (yenitlenme özelligi)

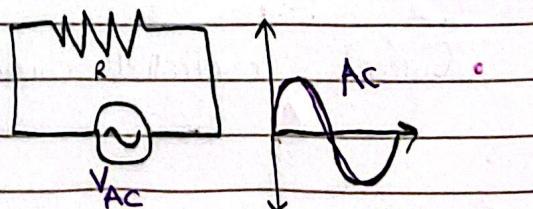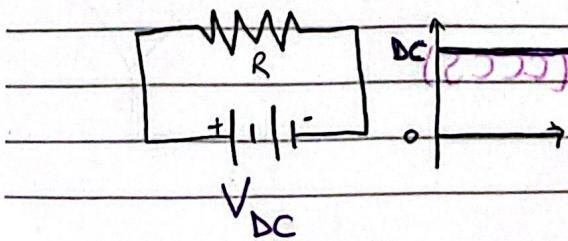- Alternating Current \rightarrow there (isn't) acronym defined for them (coba kulanırsı)



Voltage (potential difference) the electromotive force that causes charge to move. (bir yük hizmet etmek için gerekken enerji)

1 volt = 1 joule / 1 coulombs


$$V = \frac{dW}{dq}$$

$W = \text{energy} = \text{work}$

Power the change in energy as a function of time is power. (watts)

$$\rho = \frac{dW}{dq} \times \frac{dq}{dt} = V \times i = \frac{dW}{dt}$$

$$\rho = \frac{dW}{dt}$$

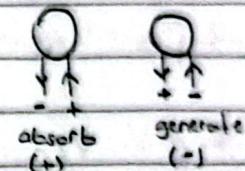

OHM'S Law voltage = current x resistance

$$V = I \cdot R$$

Volts = Amperes x Ohms


Resistivity : is a material property (ρ) dependent on the mobility of the charges. (akımın (q) hareketini sınırlendirir)

→ Resistance takes into account the physical dimensions of the material

$$\uparrow R = \rho \frac{l \uparrow}{A \downarrow}$$

l = length

A = sectional area

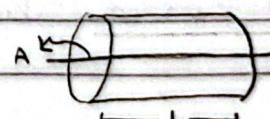

⊗ Short Circuit

if the resistor is equal to zero

$$R = 0 \Omega$$

then:

$$V = iR = i \cdot 0 = 0$$

$$V = 0$$

⊗ akım kaa dursa okun
gentim sibrdr

⊕ Open circuit

if the resistor is a perfect insulator

$$R = \infty \Omega$$

then:

$$i = \lim_{R \rightarrow \infty} \frac{V}{R} = 0$$

$$i = 0$$

⊗ gerilm olusabilir
ama akım dusur

Conductance (çelkenlik) is a reciprocal of resistance (tersi)

$$\textcircled{X} G = R^{-1} = i/v$$

$$G = A \cdot \frac{\sigma}{L}$$

\textcircled{O} σ is conductivity
which is the inverse
of resistivity (ρ)

unit for conductance is S (siemens)

$$\rightarrow \rho = iV = i(iR) = i^2 R$$

$$\rightarrow \rho = V/R \cdot V = V^2 / R$$

$$\rightarrow \rho = V/G \cdot V = V^2 / G$$

$$\rightarrow \rho = i \cdot i/G = i^2/G$$

Power

Power dissipated (sönmürmek) by a resistor is always positive

üretici \rightarrow \oplus


toretici \rightarrow \ominus

+ yönünden akım gikse üretici, akım giresse tüketici olur

Circuit terminology

\textcircled{X} NODE :

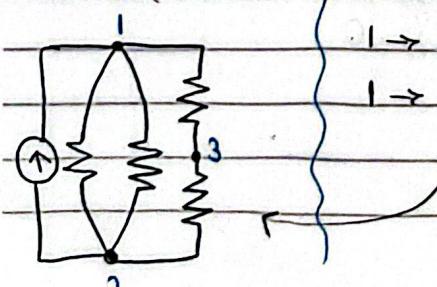point at which 2 or more elements have a common connection. (node 1)



\textcircled{X} PATH :

a route through a network, through nodes that never repeat

$$1 \rightarrow 3 \rightarrow 2$$

$$1 \rightarrow 2 \rightarrow 3$$

\textcircled{X} LOOP:


a path that starts and ends on the same node

$$1 \rightarrow 2, 1 \rightarrow 3, 3 \rightarrow 2$$

$$(3) \rightarrow 1 \rightarrow 2 \rightarrow (3)$$

\textcircled{X} BRANCH :

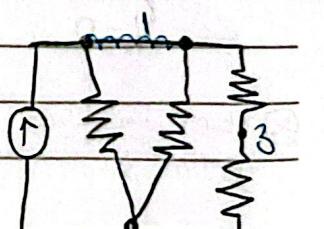a single path in a network that contains one element and the nodes at the 2 ends




Kirchhoff's Current Law (KCL)

Based upon conservation of charge, the algebraic sum of the charges within a system can not change.

$$\sum_{n=1}^N i_n = 0$$
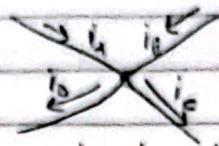
$$\sum i_{\text{enter}} = \sum i_{\text{leave}}$$




$$i_1 + i_2 + i_3 - i_4 - i_5 = 0$$

Kirchhoff's Voltage Law (KVL)

Based upon conservation of energy, the algebraic sum of voltages dropped across components around a loop is zero.


$$\sum_{m=1}^M V_m = 0$$

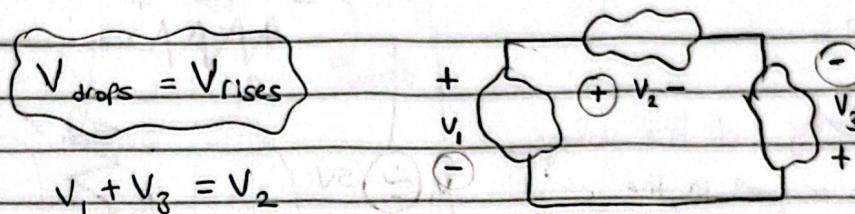The energy required to move a charge from point A to B must have a value independent of the path chosen



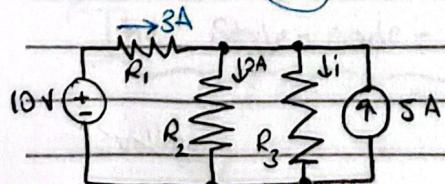
Example :

for the circuit, compute the current through R_3 . If it is known that the voltage source supplies a current of $(3A)$.



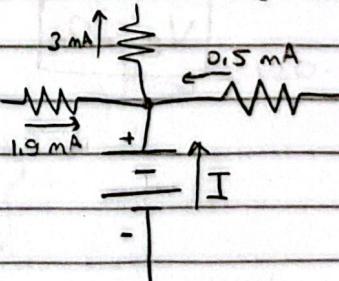Example :

Determine I the current flowing out of the voltage source.




$$1.9 \text{ mA} + 0.5 \text{ mA} + I \rightarrow \text{entering}$$

$$3 \text{ mA} \text{ Leaving}$$

$$2.4 + I = 3$$

$$I = 0.6 \text{ mA}$$

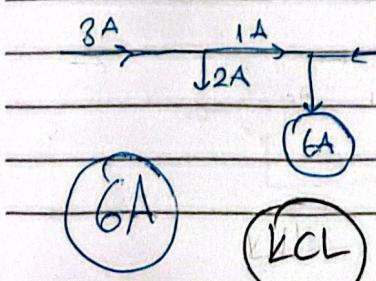

KCL

I is generating power

Example:

if voltage drops are given instead of currents,

$$V = IR$$

you need to apply Ohm's law


$$I_1 = 2V / 7k\Omega = 0.286$$

$$I_2 = 4V / 2k\Omega = 2mA$$


$$I_3 = 1.75V / 5k\Omega = 0.35mA$$

$$2 + 0.35 + I = 0.286$$

$$I = -2.06$$

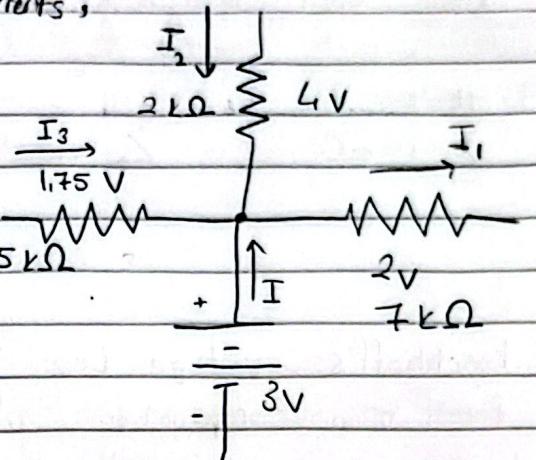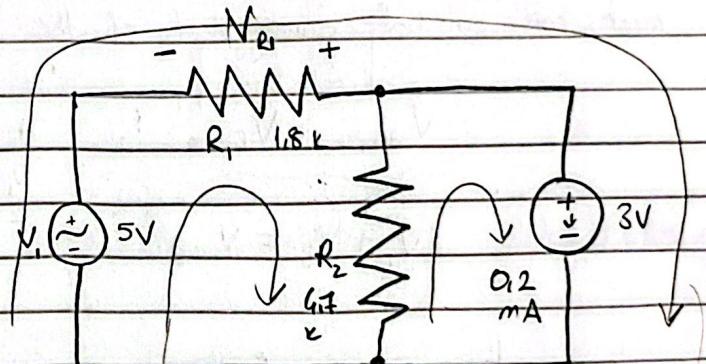Example:

- note the polarity of the voltage has been assigned in the circuit schematic.



find the voltage across R_1

$$5V + V_{R1} = 3V \rightarrow V_{R1} = 2$$

voltage

$$V_{R1} = 2$$

$$-5V - V_{R1} + 3V = 0 \rightarrow V_{R1} = 2$$

The Single-loop circuit


(for this we're gonna use KVL)

1- First step in the analysis is the assumption of reference directions for the unknown currents (given below)

2- Second step is a choice of the voltage Reference.

3- Third step is KVL
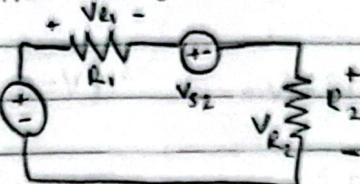
$$-V_{S1} + V_{R1} + V_{S2} + V_{E2} = 0$$



$$i = \frac{V_{S1} - V_{S2}}{R_1 + R_2}$$

Conservation of Energy

$$\sum_{\text{all elements}} P_{\text{absorbed}} = 0$$

$$P_{\text{absorbed}} = P_{\text{supplied}}$$


Example

Compute the power absorbed in each element for the circuit shown

$$120 - 30i - 2V_A + V_A = 0$$

$$V_A = -15i$$


$$120 - 15i = 0 \rightarrow i = 8$$

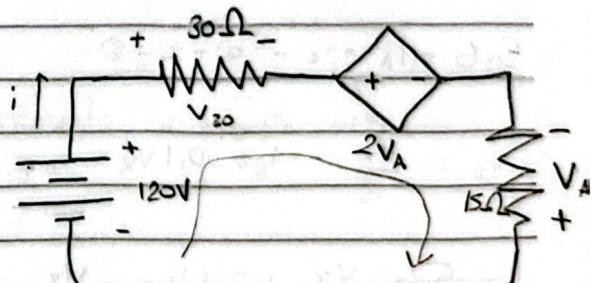

$$P_{120V} = 120 \cdot 8 = -960W$$

The Single-node-Pair Circuit

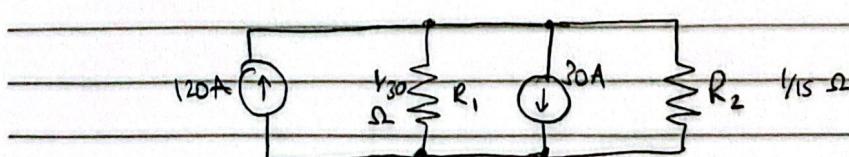
The voltage across each branch is the same as that across any other branch



ELEMENTLER PARALEL
olduğu için gerilimi-
leri eşit olur
Zorunda.

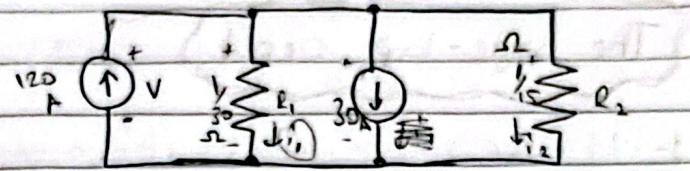*** Example:**

Find the voltage, current and Power associated with each element



$$-120 + i_1 + 30 + i_2 = 0$$

$$i_1 = 30V \quad i_2 = 15V$$

$$V = 2$$

$$i_1 = 60$$


$$i_2 = 30$$

$$P_{R_1} = 30 \cdot 2^2 = 120 \text{ W}$$

*** Example**

Find i_A , i_B and i_C

$$5,6 - i_A - i_B - i_C - 2 = 0$$

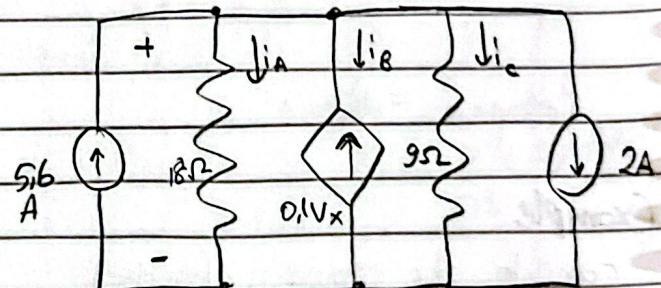


$$i_A = \frac{V_x}{18} \quad i_B = -0.1Vx \quad i_C = \frac{V_x}{9}$$

$$5.6 - \frac{V_x}{18} + 0.1Vx - \frac{V_x}{9} - 2 = 0 \rightarrow V_x = 54 \text{ V}$$


Series Circuits

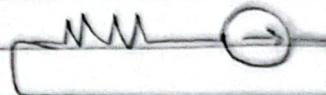all elements in a circuit (loop) that carry the same current
(ördekde same səhif elementlər seri bağdır)




Parallel Circuits

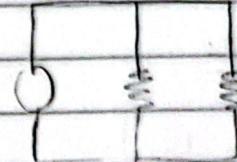all elements in a circuit that have a common voltage across them.



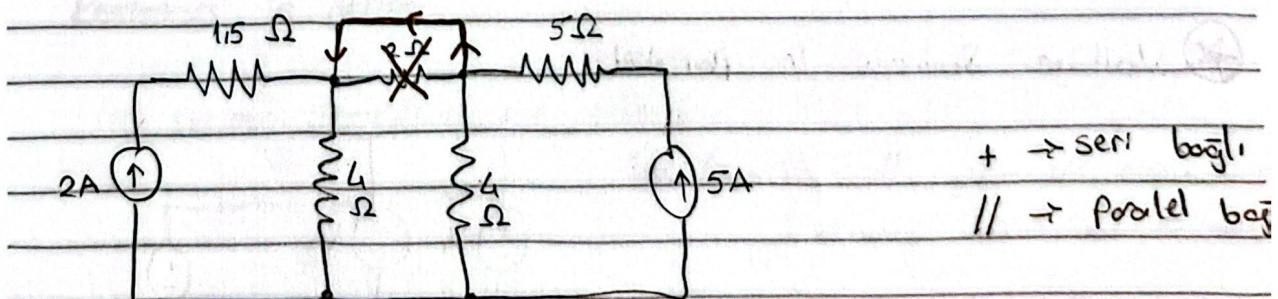Example:

in the following circuit which individual elements or groups are in Series / Parallel ?




$$((5+5) // 4) // ((1.5+2) // 4)$$

Voltage Sources in Series


→ We can replace Voltage sources in series with a single equivalent source.

→ the connection of batteries in series is common.

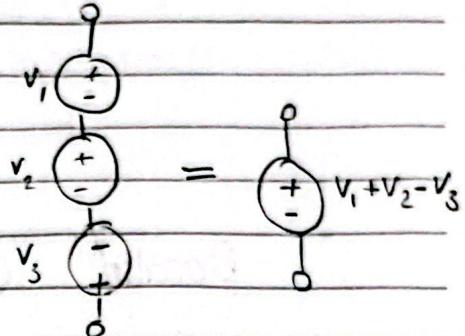→ the voltage has increased, but the maximum current for each AAA battery and for the V supply is SAME




Example:

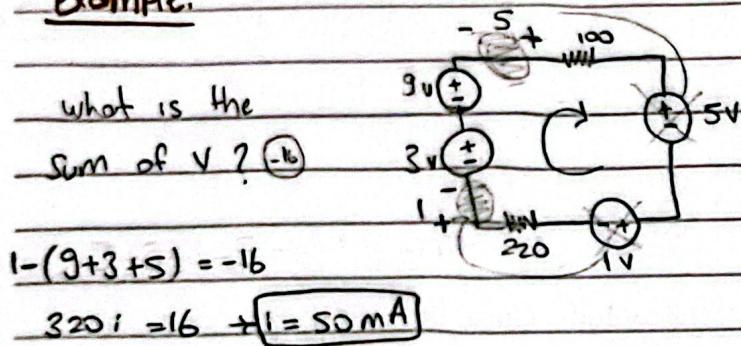

★ Voltage Sources in Parallel

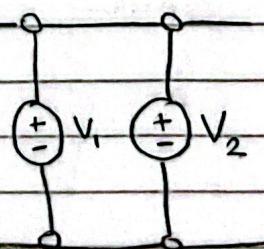
unless $V_1 = V_2$ this circuit isn't valid for ideal sources.




Current will flow from the higher source to the lower source until equilibrium is reached.

* Current Sources in Parallel

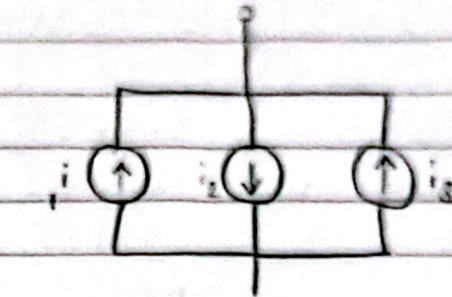
- Can replace current sources in parallel with a single equivalent source



example:

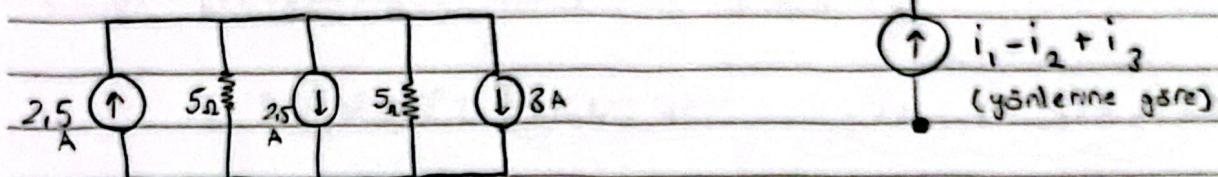

Kaynakları birleştir.

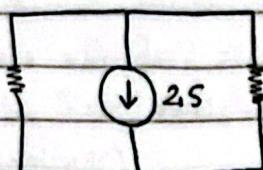

$$2.5 + 3 - 2.5 = 3 \downarrow$$




$$2.5 - 3 - 2.5 = -3 \uparrow$$

$$3 - V/5 - V/5 \Rightarrow 3 = \frac{2V}{5} \rightarrow V = 7.5 \text{ V}$$

Resistors in Series

in series, resistances are added...

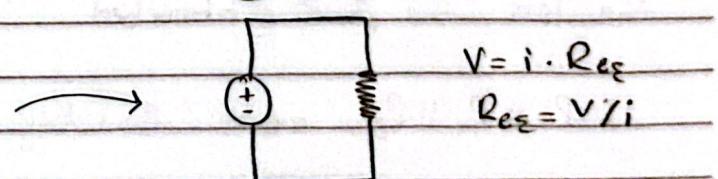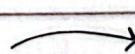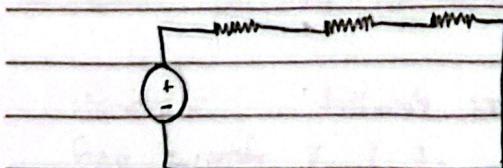
$$R_{\Sigma} = \sum_{n=1}^N R_n \quad R_1 + R_2 + R_3 = R_{\Sigma}$$



$$V = i \cdot R_{\Sigma}$$

$$R_{\Sigma} = V / i$$

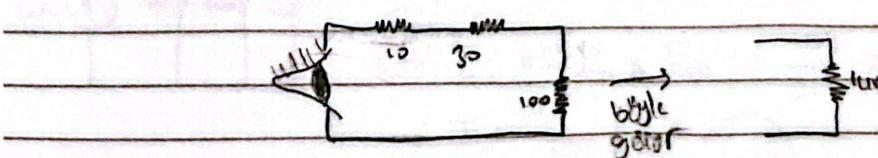It is important to realize that when a dc supply is connected it sees the total resistance seen at the connection terminals.




(*) Birnabri fiziksel öznitelikleri :

3 rankenfirmesi: dur.

$$s_{1yoh} = 0 \quad t_{1unru} = 3 \quad m_{or} = 6 \quad b_{eyoh} = 9$$

$$k_{ahver} = 1 \quad s_{2y} = 4 \quad m_{or} = 7$$
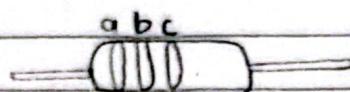
$$k_{urm. g_1} = 2 \quad y_{c=1} = 5 \quad g_{r_1} = 8$$



Renkler (a,b) $\times 10^6$ ohm seklinde okunur

(*) $P_E = P_{E_1} + P_{E_2} + P_{E_3}$ } $P = V \cdot I = I^2 R = V^2 / R$

Resistors in Parallel:

→ for resistors in parallel, the reciprocals of the resistances sum to 1 / the equivalent

$$(R_{eq})^{-1} = 1/R_1 + 1/R_2 + 1/R_3 \quad i_s = i_1 + i_2 + i_3 + \dots + i_n$$

- Always keep in mind that ohmmeters can never be applied to a live circuit


- in parallel resistive network, the larger the resistor, the less the power absorbed

- $R_1 \parallel R_2 \parallel R_3$ means that they are parallel

- illetkenlikte paralellik = Diferansiyel Seri

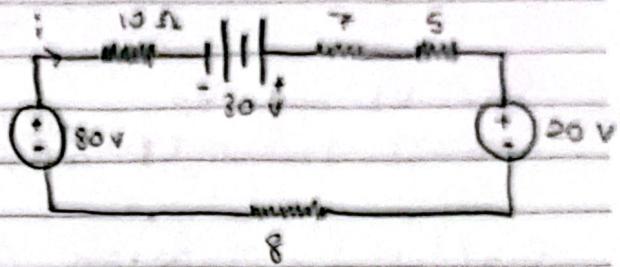Example:

use resistance and source combinations to determine the current i and the power delivered by the 80 V source



$$20 - 80 - 30 = -90 \rightarrow \text{volt}$$

$$10 + 7 + 5 + 8 = 30 \rightarrow R$$

$$V = I \cdot R$$

$$-90 = 30 \cdot i$$

$$P = I \cdot V$$

$$-90 = 3 \cdot 80$$

$$\underline{i = 3\text{ A}} \quad \underline{P = 240 \text{ W}}$$

Voltage Division:

- All resistors in Series share the same current

- the Source voltage V is divided among the resistors in direct proportion to their resistances. (Potansiyel farklı orantılı bir şekilde dirençlere bölünür)

Sadece DC (direct current) için değil AC (alternating current) için de geçerlidir. (Geri dönüşü özelligi hep geçerli)

Current Division:

- All resistors in parallel share the same voltage

- The total current I is shared by the resistors in inverse proportion to their resistances

Example:

Find currents I_1, I_2, I_3

in the circuit. $2,18 \quad 1,09 \quad 0,727$

$$I_{\text{in}} \uparrow \quad \begin{array}{|c|c|c|} \hline & i_1 & i_2 & i_3 \\ \hline 200 & & 400 & 600 \\ \hline \end{array} \quad R_{\Sigma} = \frac{1}{\frac{1}{200} + \frac{1}{400} + \frac{1}{600}} = \frac{1}{11/1200} = 109 \Omega$$

$$I_1 = \frac{R_{\Sigma}}{R_1} \times I_{\text{in}} = \frac{109}{200} \times 4 = 2,18$$


$$I_2 = \frac{109}{400} \times 4 = 1,09 \quad I_3 = \frac{109}{600} \times 4 = 0,727$$

Subject:

Date:

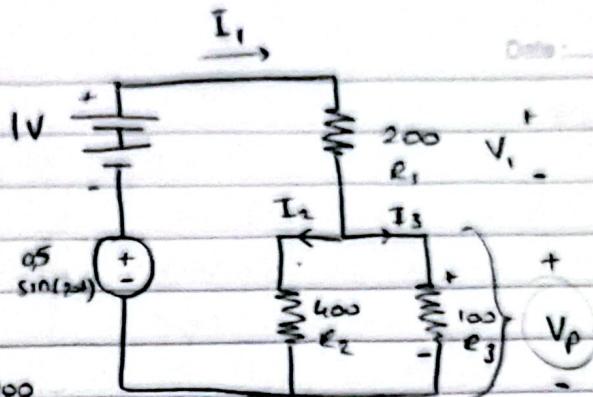Example:Find V_1 and V_p Find I_L , I_2 and I_3

$$R_{eq} = \left(\frac{1}{200} + \frac{1}{100} \right)^{-1} = \frac{400}{3} = 80 + 200$$



$$R_{eq} = 280 \Omega$$

$$V_{top} = 1V + 0.5 \sin(20t)$$

$$I_1 = \frac{V_{top}}{R_{eq}} = \frac{1V}{280} + \frac{0.5 \sin(20t)}{280} = 3.57 \text{ mA} + 1.79 \text{ mA} \sin(20t)$$

$$V_1 = R_1 \cdot I_1 = 200 \cdot (3.57 + 1.79 \text{ mA}) = 0.714 \text{ V} + 0.357 \text{ V} \sin(20t)$$

$$V_p = R_{eq1} \cdot I_1 \rightarrow 80 \cdot I_1 = 0.28 \text{ V} + 0.143 \text{ V} \sin(20t)$$

$$I_2 = \frac{R_{eq}}{R_2} \cdot I_1 = \frac{280}{400} \cdot I_1 = 0.7 \cdot I_1 = 0.714 \text{ mA} + 0.357 \text{ mA} \sin(20t)$$

$$I_3 = R_{eq}/R_3 \cdot I_1 = 280/100 \cdot I_1 = 2.86 \text{ mA} + 1.43 \text{ mA} \sin(20t)$$

Önemli: formüller

$$V_n = \frac{R_n}{R_{eq}} \cdot V_{total}$$


$$I_m = \frac{R_{eq}}{R_m} \cdot i_{total}$$

nV

S

Wye and Delta Networks

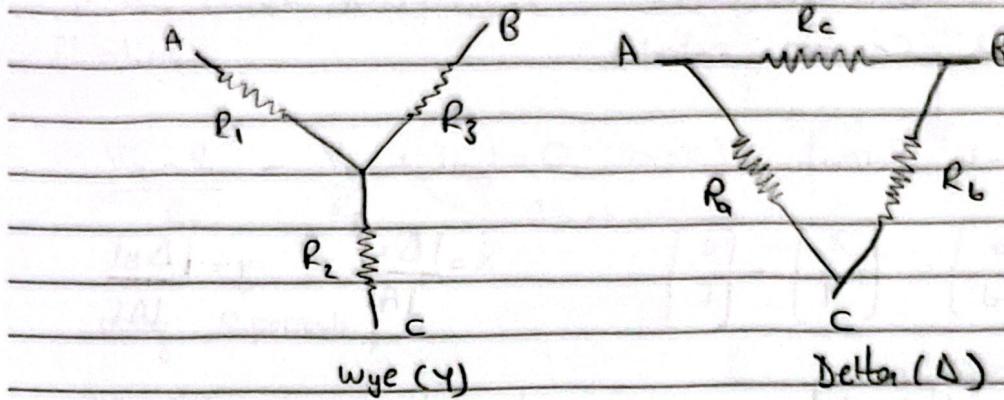→ 3 terminal arrangements - commonly used in power systems



* it must be ;

$$\rightarrow R_1 + R_2 = R_A$$

$$\rightarrow R_1 + R_3 = R_C$$

$$\rightarrow R_2 + R_3 = R_B$$

* wye windings provides better torque at low rpm


* delta windings generates better torque at high rpm

Bridge Circuits

→ Measurement of the voltage

V_{AB} is used in sensing and full-wave rectifier circuits

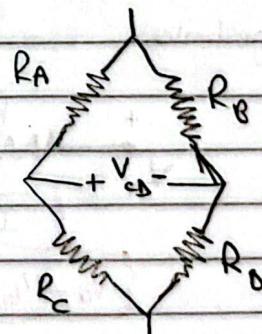* if $R_A = R_B = R_C = R_D$, $V_{AB} = 0V$



* Sesör olusturmak bu şekilde ortamdağı sartlardan minimum etkileşim hizasına bir sağlam elde ederiz...

Nodal and Mesh Analysis

dogru

cevri

~ mathematical preliminaries ~

→ tozit esitsizlik ve denklemler

→ determinant (cramer methodu) :

$A \cdot x = b$ format

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \cdot \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} e \\ f \end{bmatrix} \quad x = \frac{|\Delta_x|}{|A|} \quad y = \frac{|\Delta_y|}{|A|}$$

$$|\Delta_x| = \begin{vmatrix} e & b \\ f & d \end{vmatrix} \quad |\Delta_y| = \begin{vmatrix} a & e \\ c & f \end{vmatrix} \quad |A| = \begin{vmatrix} a & c \\ b & d \end{vmatrix}$$


* Nodal Analysis:

Technique to find currents at a node using Ohm's Law and the potential differences between nodes.

→ first, determine the node voltages (referenced to ground)

→ Second, calculate the currents

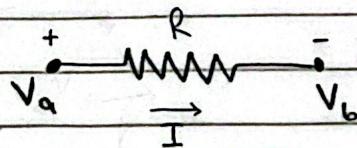* dogru gerilimler: überinden gider! (akim (KCL) denklemleri ile)



$$V_a - V_b = I \cdot R \quad \text{and} \quad I = (V_a - V_b) / R$$


→ Current flows from a higher potential to a lower potential in a resistor

Example:

Determine the current

flowing left to right through the 15 ohms

resistor

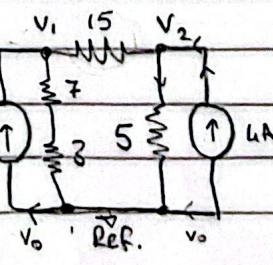

$$I = \frac{V_1 - 0}{10} + \frac{V_1 - V_2}{15}$$

$$V_1 = 20$$

$$I = \frac{V_2 - V_0}{5} + \frac{V_2 - V_1}{15}$$


$$V_2 = 20$$

$$6V_2 - V_1 = 60 \quad 5V_1 - 2V_2 = 60$$

Q) nodal analysis with Supernodes:

A floating source is a problem for the Nodal Analysis.

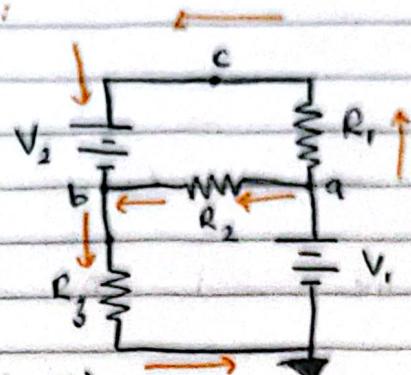In this circuit, battery V_2 is floating.



$$\frac{V_a - V_b}{R_2} - \frac{V_b}{R_3} + i_{V_2} = 0 \quad (V_a = V_1)$$

? It's not a resistance?

Using Supernode;

$$\frac{V_1 - V_b}{R_2} - \frac{V_b}{R_3} + \frac{V_1 - (V_b + V_2)}{R_1} = 0 \quad \text{yani} \quad V_c = V_b + V_2$$


Example

$$14A = \frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2}$$

$$0.5V_x = \frac{V_2 - V_2 + iV_y}{2}$$

Super node
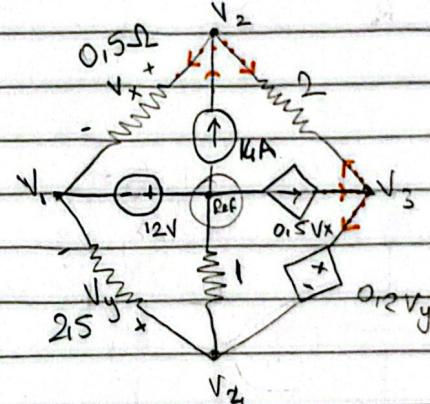
$$\frac{V_u - 0}{1} + \frac{V_u - V_1}{2.5}$$



$$V_1 = -12V \quad V_2 - V_u = 0.2V_y \quad 0.5V_x = (V_2 - V_1) \cdot 0.5 \quad V_y = V_1 - V_u \cdot 2.5$$

$$5V_2 - 4V_1 - V_3 = 28A \quad (7V_4 - V_1) \cdot 2 + 5V_3 - 5V_2 = V_2 - V_1 \cdot \frac{1}{2}$$

$$28V_4 - 4V_1 + 10V_3 - 10V_2 = V_2 - V_1$$

$$V_2 - V_u = (V_1 - V_4) \cdot \frac{5}{2}$$

$$28V_4 - 3V_1 + 10V_3 - 11V_2 = 0$$

$$2V_3 - 2V_u = 5V_1 - 5V_4$$

$$3V_4 + 2V_3 = 5V_1$$

$$3V_u = -60 - 2V_3 - 60$$

$$28V_4 + 10V_3 = 3V_1 + 11V_2$$

-36

$$V_u = \frac{-60 - 2V_3}{3}$$

$$V_2 = -6 \quad V_3 = 0 \quad V_4 = -2$$

$$\begin{aligned}
 3I_2 - 3I_2 &= 62V \\
 -3I_1 + 2I_2 &= 30V \\
 \hline
 12I_2 &= 72 \\
 I_2 &= 6A \\
 I_1 &= 4A
 \end{aligned}$$



Subject :

Date :


Mesh Analysis :

- to find voltage drops within a loop using currents that flow within the circuit and Ohm's Law.

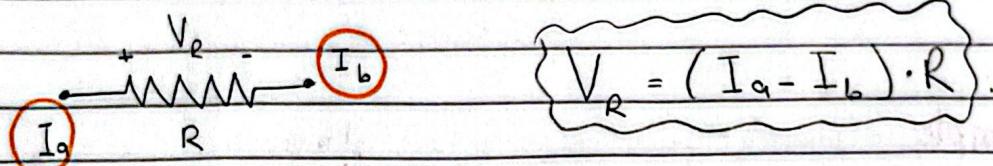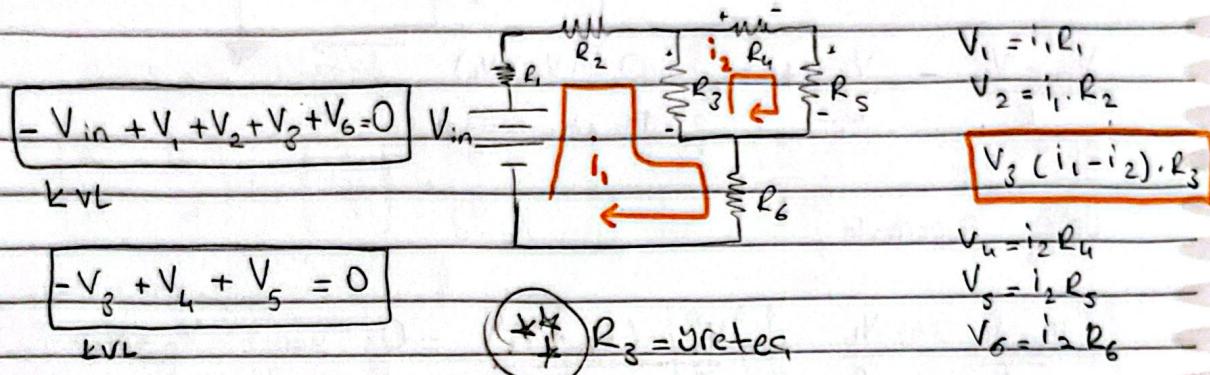- Mesh: the smallest loop around a subset of components in circuit



Example :

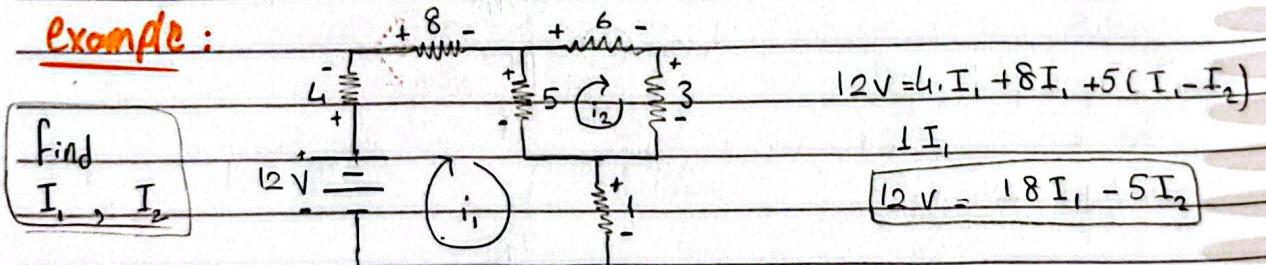

$$12V = 18I_1 - 5 \cdot \frac{5}{14} I_2$$

$$5(I_3 - I_2) = 6I_2 + 3I_2$$

$$5I_1 = 14I_2$$

$$7I_1 = I_1$$

$$26I_2 = I_2$$


Example :

Determine the power supplied by the 2 V source

$$P = I \cdot V$$

$$5V = 4i_1 + 2i_2 - 2V$$

$$-3V = 5i_2 - 2(i_1 - i_2)$$

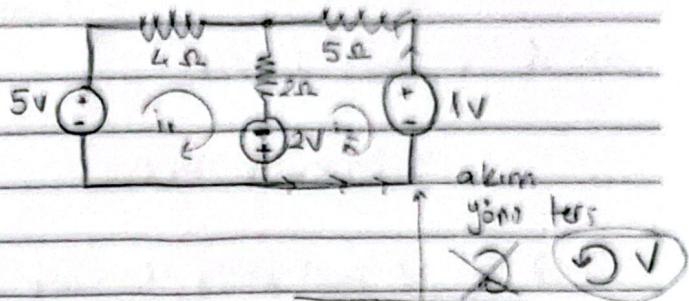


$$\begin{aligned} 7V &= 6i_1 - 2i_2 \\ (-3V) &= 7i_2 - 2(i_1 - i_2) \end{aligned}$$

$$-2V = 19i_2$$

$$\begin{aligned} i_2 &= -0.1053 \\ i_1 &= 1.132 \end{aligned}$$

$$P = -2 \cdot 1.132 \cdot 7 = -21.474 \text{ W}$$

~~* Mesh Analysis with Supermeshes :~~

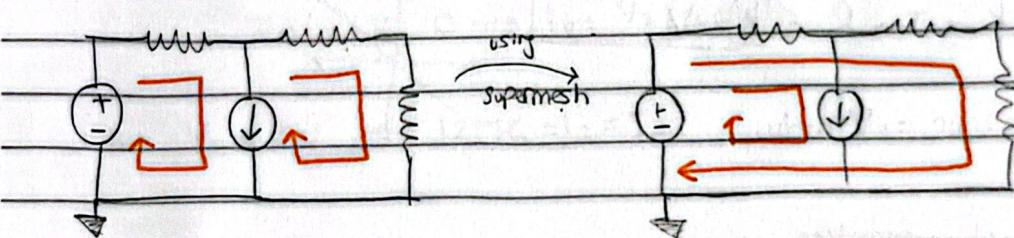

Supermesh: a mesh that contains multiple meshes with a shared current source

Example :


Determine the current i_3 as labeled in the circuit

$$7V = 1(i_1 - i_2) + 3(i_2 - i_3) + 1i_3$$

$$i_1 - i_2 = 2i_2 + 3(i_2 - i_3)$$

$$-i_1 + 6i_2 - 3i_3 = 0$$

$$i_1 - i_3 = 7$$

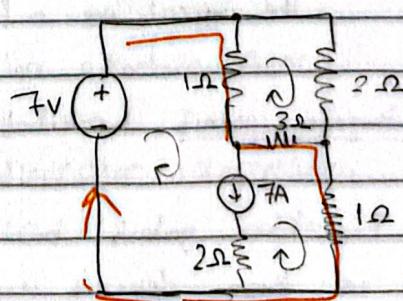

Linearity

→ if x is doubled,

$$y = f(2x) = 2f(x)$$


→ if x is multiplied by any constant, a

$$y = f(ax) = af(x)$$


* then the system is linear

(*) if the current is increased by a constant k , then the voltage increases correspondingly by k ;

$$[k] \times I + R = [k] \times V$$

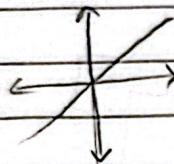

→ Diode characteristics

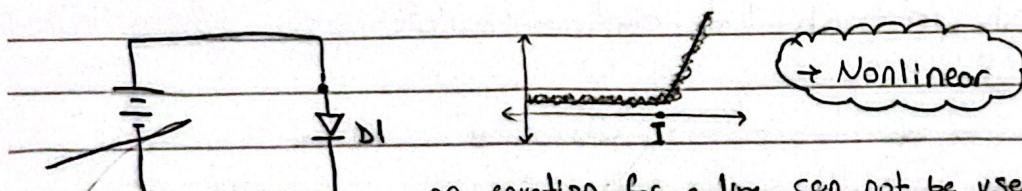

an equation for a line can not be used to represent the current as a function of voltage

Superposition

* Gerilim kaynakı yalnız bırakıldığında, akım kaynakları açık devre yapılır.

* Akım kaynakları yalnız bırakıldığında, gerilim kaynakları devre den ayrılmır ve kısa devre yapılır

Summary : The property is used to separate contributions of several sources in a circuit to the voltages across and the currents through components in the circuit.

* Superposition

~~Example~~

For the circuit, find I_o when $V_s = 12V$ and $V_s = 24V$.

$$V_s = 6i_1 + 2i_1 + 4i_1 - 4i_2 = 12i_1 - 4i_2$$

$$V_s + 3(2i_1) = 4i_2 - 4i_1 + 8i_2 + 4i_2$$


$$\rightarrow V_s = 16i_2 - 10i_1 = 12i_1 - 4i_2$$

$$12i_1 - 4i_2 = -V_s \quad | \quad 2i_1 + 12i_2 = 0$$

$$+ 16i_2 - 10i_1 = V_s \quad | \quad i_1 = -6i_2$$

$$\rightarrow 16i_2 - 10 \cdot (-6i_2) = V_s$$
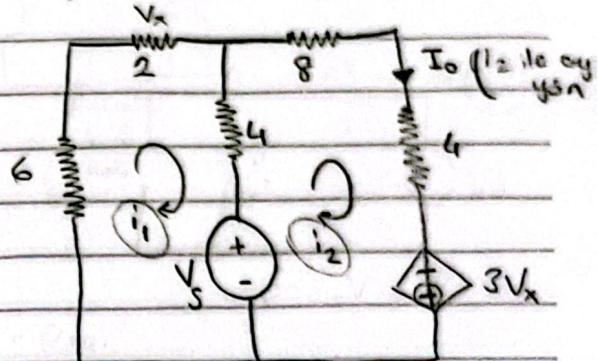
$$76i_2 - V_s = 0 \rightarrow i_2 = V_s / 76$$



$$\text{when } V_s = 12V \rightarrow 12/76 = i_2 = I_o \quad \text{when } V_s = 24V \rightarrow 24/76 = i_2 = I_o$$

Superposition

* voltage sources should be replaced with short circuits

* current sources should be replaced with open circuits


* bağımlı kaynak varsa bunları akıtmayıza *

→ kaynakları çıkarsak da dirençler üzerindeki ilk etyeni edilen polarization değişir

~~Example~~


Date: _____

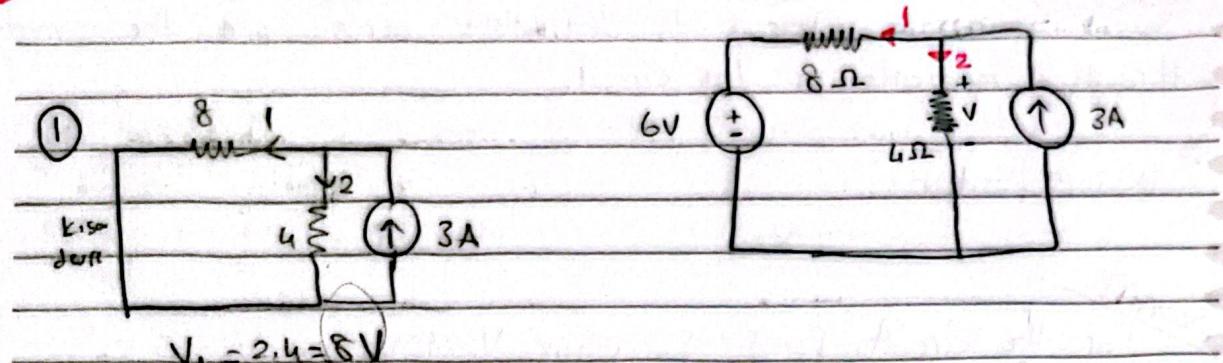Use the superposition theorem to find V in the circuit.



~~Example~~

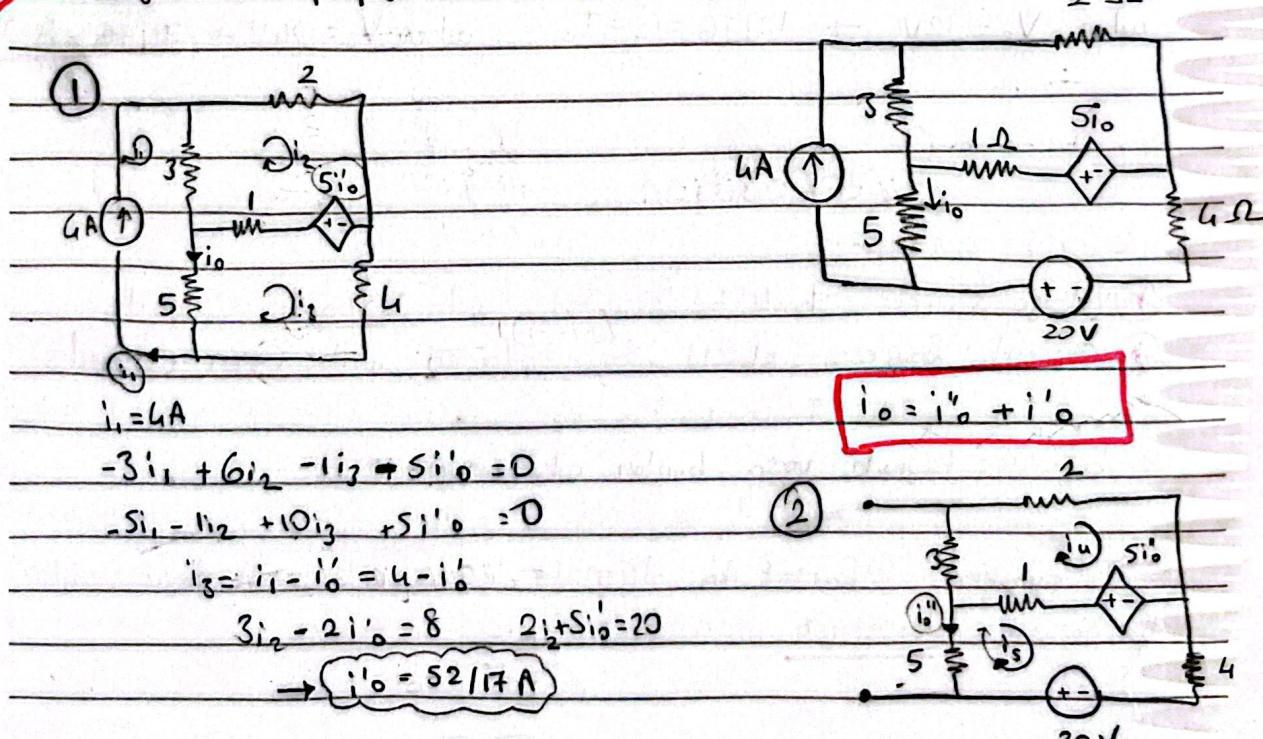using the superposition theorem, find i_o in the circuit.



$$i_o = \frac{52}{17} + \frac{(-60)}{17}$$


$$i_o'' = \frac{-60}{17} = 0 = 6i_4 - 4i_o'' \quad \left\{ \begin{array}{l} 6i_4 - i_5 - 5i_o'' = 0 \\ -20 = i_4 + 5i_o'' \end{array} \right. \quad -20 = 40i_s + 5i_o'' - i_4 = 0$$

$$i_o = -8/17$$

$$i_s = -i_4$$

Source transformation: Devreyi daha sade bir şekilde göstermek için kaynaklar arasıda dönüşüm yapmakta?

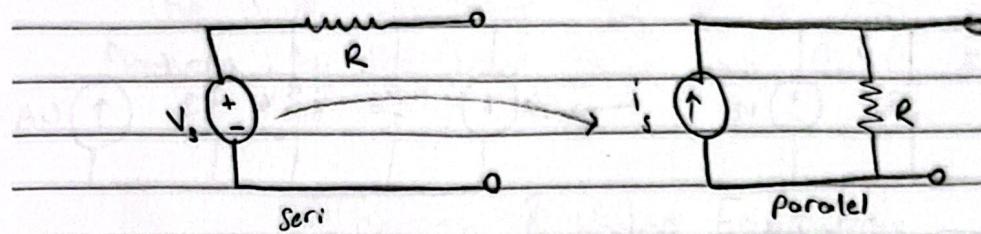
A source transformation is the process of replacing a voltage source V_s in series with a resistor R by a current source i_s in parallel with a resistor R .



* Voltage Sources:


- Ideal

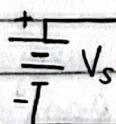- an ideal voltage source has no internal (internal) resistance
→ no limit (producing current)



- Real

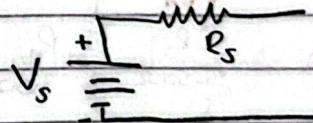
- is modeled as an ideal voltage source in series with a resistor.
→ there are limits



* Current Sources:


- Ideal

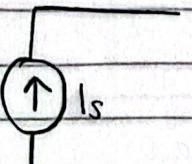- no internal resistance
→ no limit (power)



- Real

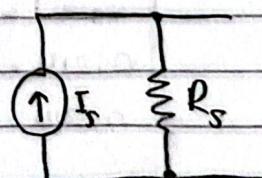- ideal current source + parallel with resistor.
→ have limits (volt and current)



$$P_{Vg} = 10 \text{ mW}$$

$$0.214 \cdot (5 - 0.714) = P_{Rs}$$


$$0.214 \cdot 0.714 = P_L$$

$$P_{Vg} = P_L + P_{Rs}$$

$$V_L = I_L \cdot R_L = 0.714 \cdot 300 = 0.214 V$$

$$I_L = \frac{800 + 50}{50} \cdot I_S = \frac{850}{50} \cdot 0.714 = 5 / \text{A}$$


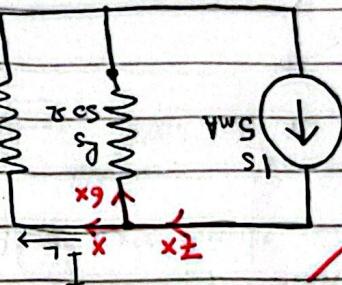
Circuit below
to replace I_S and R_L in the
Find an equivalent Voltage Source



~~example~~


$$V_o = \frac{10}{8+2} \cdot 2 = 3.2 \text{ V}$$

$$V_o = 8 \cdot 0.4 = 3.2 \text{ V}$$

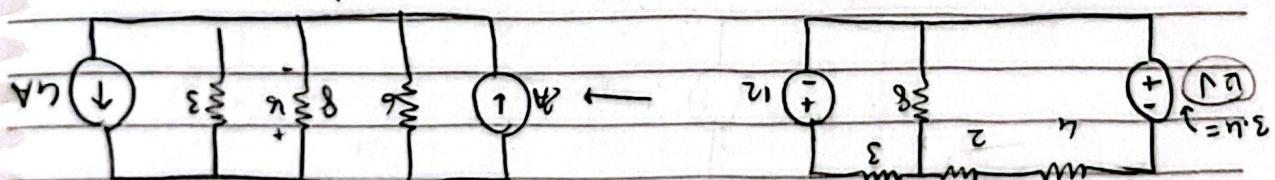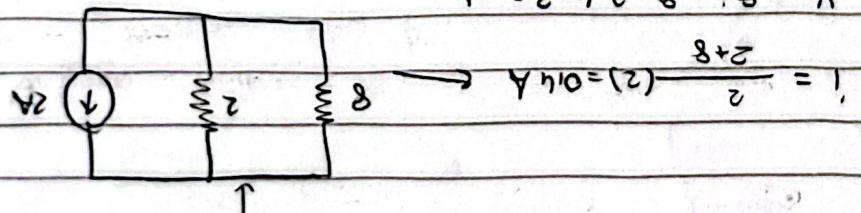

diode VD
diode parallel

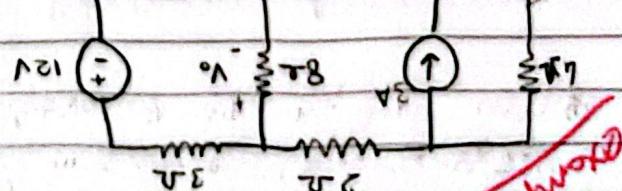the circuit.
solution to find V_o in
use Source Transformation.



~~example~~
Subject

Diode forward biased




Summary an equivalent circuit is a circuit where the voltage across and the current flowing through a load R_L are identical

- if the shunt resistor decreases \rightarrow current increase. ($\frac{R_{\text{shunt}}}{R_{\text{shunt}} + R_s}$)
- if the series resistor increases \rightarrow voltage increase ($\frac{R_{\text{shunt}}}{R_{\text{shunt}} + R_s}$)

The power dissipated by R_L is 1/50 of the power produced by the ideal source when $R_L = R_s$



-Thevenin & Norton Equivalents -

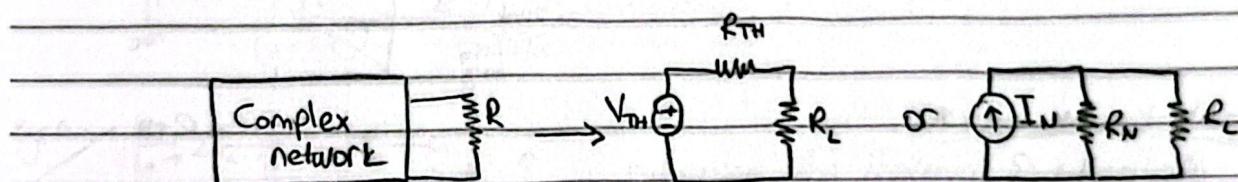Any linear circuit network at two terminals may be replaced with a Thevenin (V_{TH}, R_{TH}) or a Norton (I_N, R_N)




1- Thevenin equivalent,

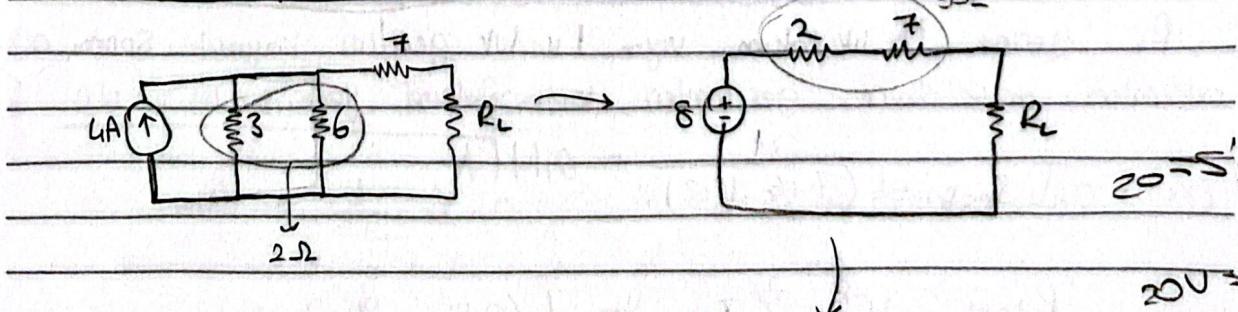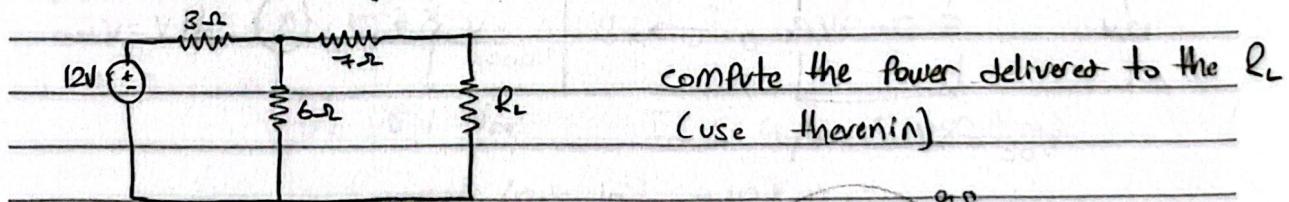use repeated source transformations to arrive at a single voltage source in series with a single series resistance




$$P_L = \left(\frac{8}{9+R_L} \right)^2 R_L \quad V_{TH} = 8 \text{ V} \quad R_{TH} = 9 \Omega \quad 50\%$$

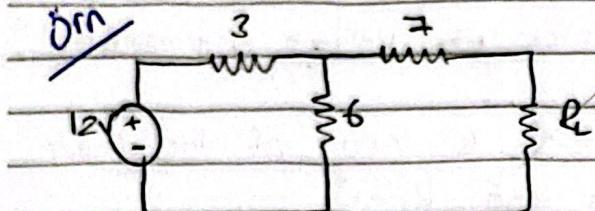
Method - 2 : Open the load and determine the open-circuit voltage, then short the load and determine the short-circuit current.



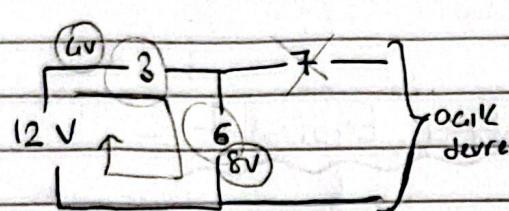Determine the Thévenin eq.
using method 2.



$$V_{TH} = 8V$$

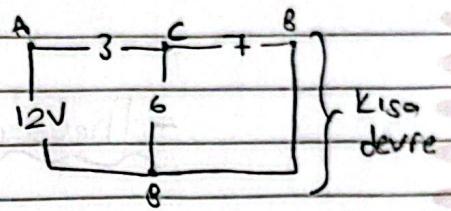

$$\text{short circuit } R_{TH} = ?$$




$$9\Omega = R_{TH}$$

* bağımlı kaynak varsa *

Method - 3

→ when the circuit includes dependent sources.

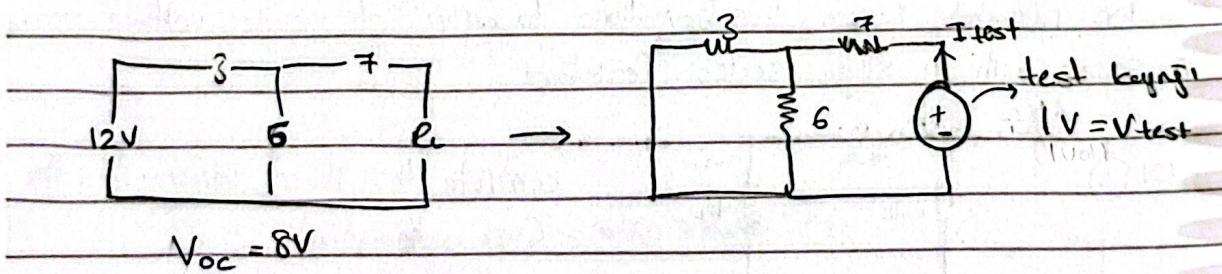→ open the load and deactivate all independent sources



$$V_{OC} = 8V$$


R_L yerine 1A akım veya 1V gerilim kaynat. Sonra eski akımları açık devre, gerilimleri kısır devre yapınız.

$$I_{test} = \frac{1}{(7+6||3)} = 0.111A$$


$$R_{test} = V_{test} / I_{test} = 1 / 0.111 = 9\Omega$$

Subject :




Date : 10/10/2023

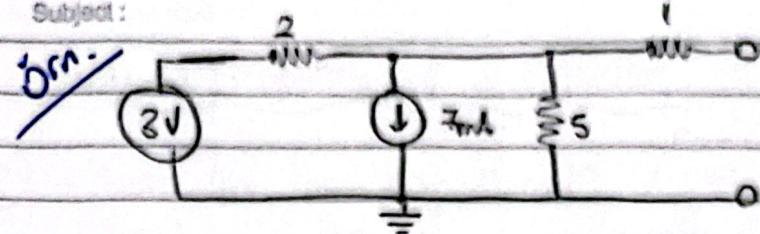

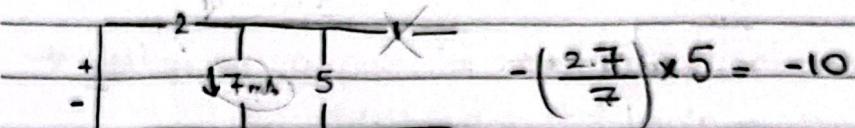Determine the Thévenin and Norton equivalents of the circuits.



$$2.14 - 10 = (-7.86) V_{TH}$$

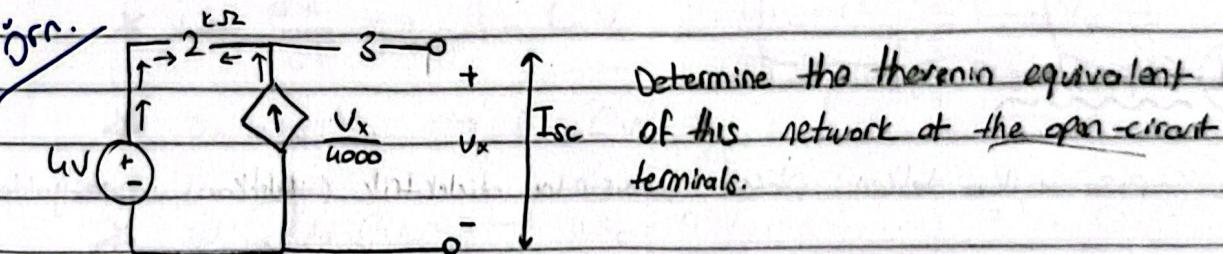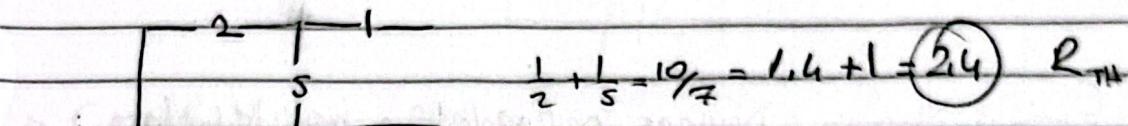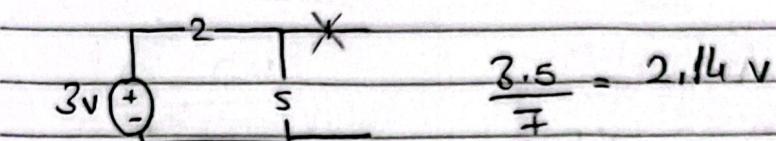

Determine the Thévenin equivalent of this network at the open-circuit terminals.

$$-6 + 2 \cdot 10^3 \left(-\frac{V_x}{4000} \right) + 3 \cdot 10^3 \cdot 0 + V_x = 0$$

$$V_x = 8 \text{ V} = V_{oc} \quad I_{sc} = 6 / 5 \cdot 10^3 = 0.8 \text{ mA}$$

$$R_{TH} = 8 / 0.8 \cdot 10^{-3} = 10 \text{ k}\Omega$$

Maximum Power Transfer

$$\text{Max. val.} \rightarrow \frac{d}{d R_L} P_L = 0 \quad \text{if } R_L = R_S \rightarrow \frac{d}{d R_L} P_L = 0 \text{ (max)}$$

Max power delivered to the load


when the load resistance = Thévenin resistance

$$P_L = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$

$$R_L = R_S \quad \text{yso}$$


Subject :

Date :

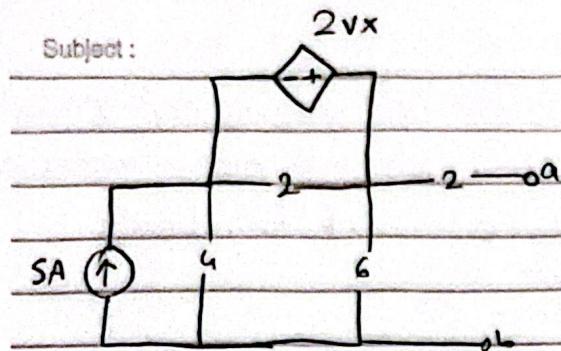

find the Thvenin equivalent

başlıklı kaynak var → akım testi :

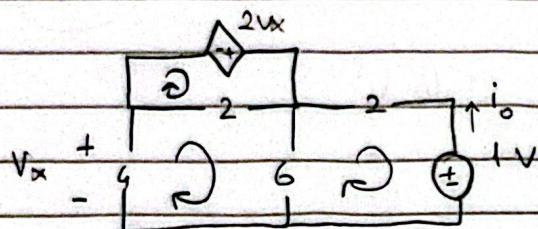: Energy Storage Devices ~ Capacitors and inductors :(1) Capacitors : gerilim saklayıcı

yapısı : iki metten plaka arasındaki dieltrik (yolikta) metayalden oluşur.

$$C = \epsilon \cdot \frac{A}{d}$$

$\epsilon = \epsilon_r \epsilon_0$
 $\epsilon_r = \text{relative constant}$
 $\epsilon_0 = \text{vacuum permittivity}$


plate Area (A)
yolikta
media
d

yüzeyalı, epsilon ile deðri, d ile ters orantılı.

a - Nonpolarized (Kutupsuz) capacitors:

paper, ceramic

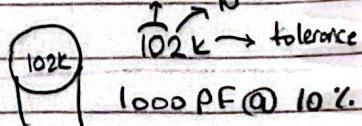
Tolerance on capacitance values is very large



1000 pF @ 10%.

b - Electrolytic (Kutuplu) capacitors : the negative terminal must always be at a lower voltage than the positive terminal

Aluminum

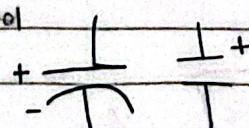

Electrical Properties of a Capacitor


* → Acts like an open circuit at steady state (Dayum) when connected to a DC voltage or current source

→ Voltage on a capacitor must be continuous (sorek, gerikan gantung)

Energy Storage

$$Q = CV$$

Coulomb = Farad. Voltage

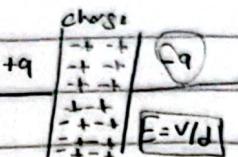

$$C = \frac{Q}{V}$$

$$V = Ed$$

not yet
mass-f

→ Current - Voltage Relationships

$$i_c = \frac{dq}{dt} \rightarrow q = C V_c$$

$$i_c = C \frac{dV_c}{dt}$$

$$V_c = \frac{1}{C} \int i_c dt$$

$$P_c = i_c \cdot V_c \rightarrow P_c = C V_c \cdot \frac{dV_c}{dt}$$

$$W_c = \frac{1}{2} C V_c^2 \rightarrow W_c = \frac{q^2}{2C}$$

$$U = \frac{1}{2} C V^2$$

Time Constant

→ Charging


$$V(t) = V_c (1 - e^{-t/\tau})$$

→ Discharging

$$V(t) = V_c e^{-t/\tau}$$

$$\tau = RC$$

→ Capacitors in parallel :

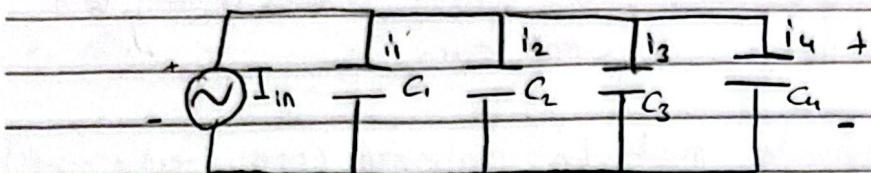

paralelde normal toplama yapılır.

$$- C_{eq} = C_1 + C_2 + C_3 + C_4$$

→ in Series :

$$- C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} \right)^{-1}$$

Summary


- An ideal capacitor acts like open circuit when a DC volt. or current has been applied for at least 5T
- Must be continuous.

(2) inductors : (akım) deflame

the flow of current through an inductor creates a magnetic field
(right hand rule)

- akım sürekli olmalı -

* sevi olduğunda short circuit +

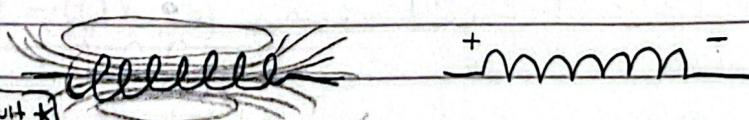

L , inductance, has the units of Henries (H) $1H = 1V \cdot s/A$

$$V_L = L \frac{di}{dt} \quad i_L = \frac{1}{L} \int_{t_0}^{t_1} V_L dt$$

→ inductors in Series

$$\bullet L_1 + L_2 + L_3 + L_4$$

→ In Parallel

$$\bullet \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} \right)^{-1}$$

Power and Energy

$$\rightarrow P_L = V_L \cdot i_L = L i_L \int_{t_0}^t i_L dt \quad \rightarrow W = \int L \frac{di_L}{dt} dt = L \int i_L di_L$$

Calculations of L

$$\rightarrow L = \frac{N^2 \mu A}{l} = \frac{N^2 \mu_r \mu_0 A}{l}$$

N: the number of turns of coil

A: sectional area

μ : mobilité

l: length


Wire

unfortunately, even bare wire has inductance

$$L = l \left[\ln \left(\frac{4l}{d} \right) - 1 \right] (2 \cdot 10^{-7}) H$$


d: diameter of the wire

Operational Amp

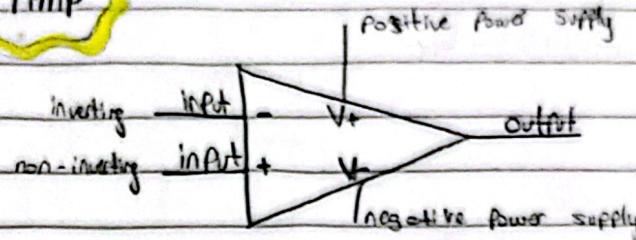

the potential difference between the 2 inputs is \rightarrow zero

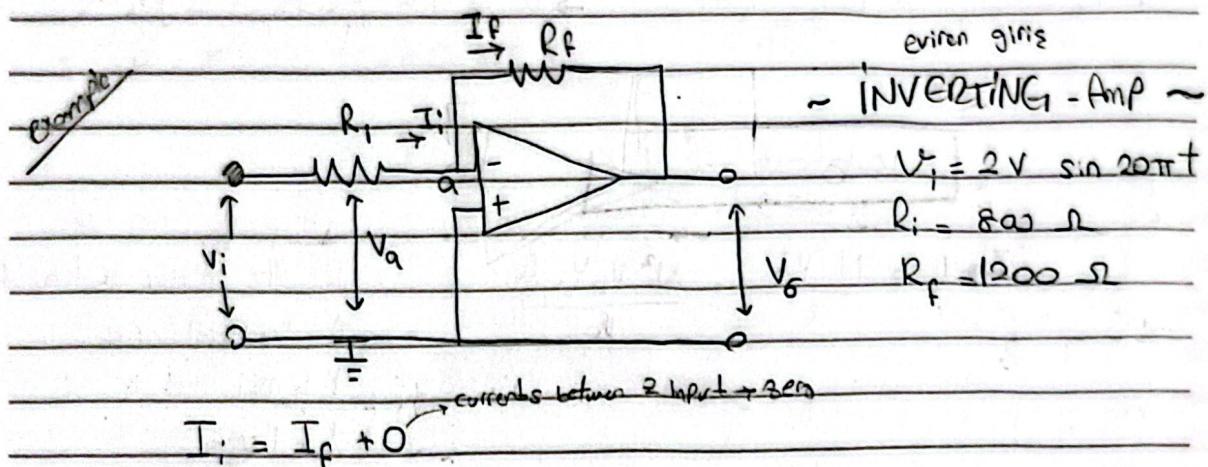
the currents at the 2 inputs is \rightarrow zero




$$V_a - V_i = \frac{V_o - V_a}{R_f} \rightarrow V_a = 0 \rightarrow \text{ground}$$


$$-\frac{V_i}{R_i} = \frac{V_o}{R_f} \rightarrow -V_i = V_o \left(\frac{R_i}{R_f} \right) \quad | \quad V_o = -V_i \left(\frac{R_f}{R_i} \right)$$
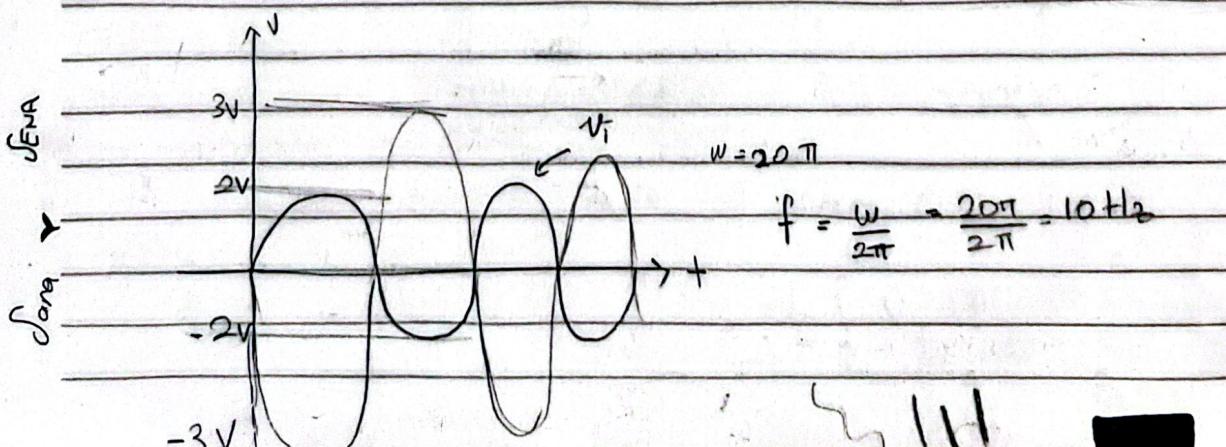
$$V_o = -2 \text{ V} \sin(20\pi t) \cdot \frac{1200}{800} = -2 \cdot \frac{3}{2} \sin(20\pi t) = -3 \text{ V} \sin(20\pi t)$$



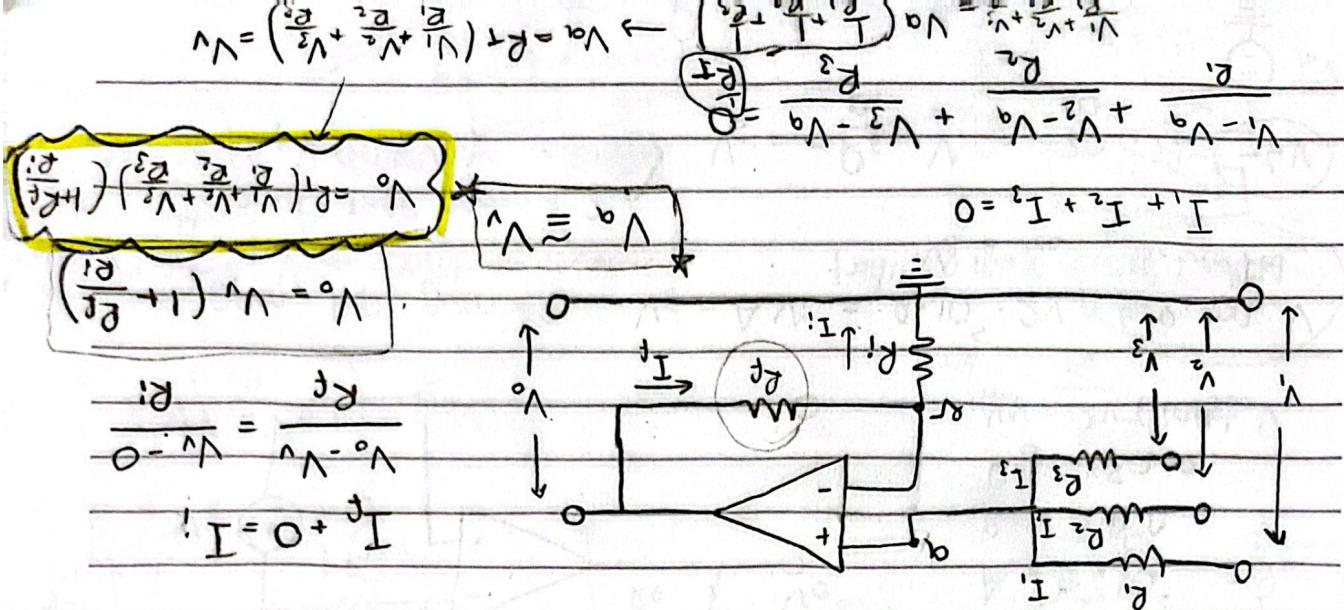



Summing amplifier - OA - Inverting

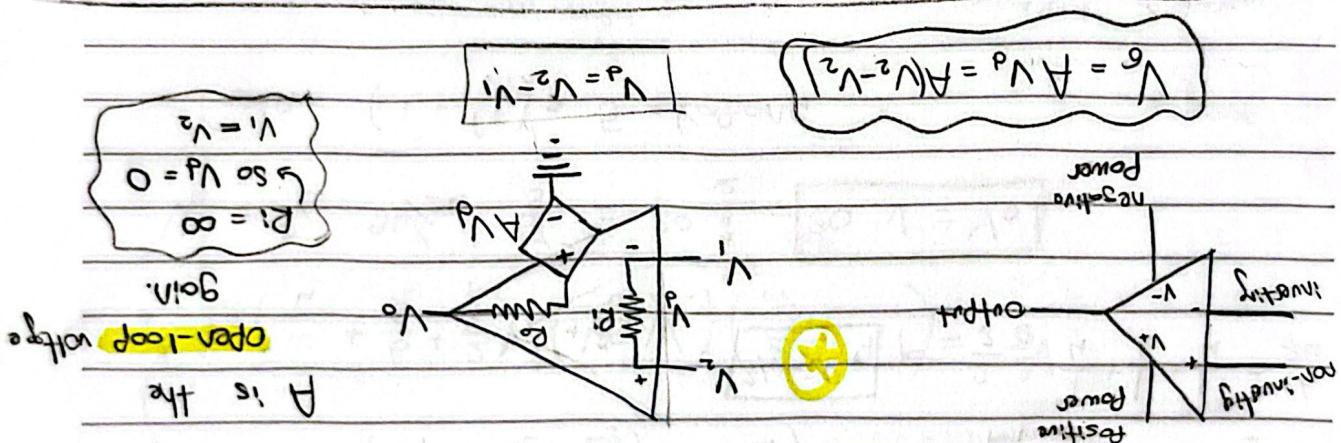

Non-ideal OP-Amp
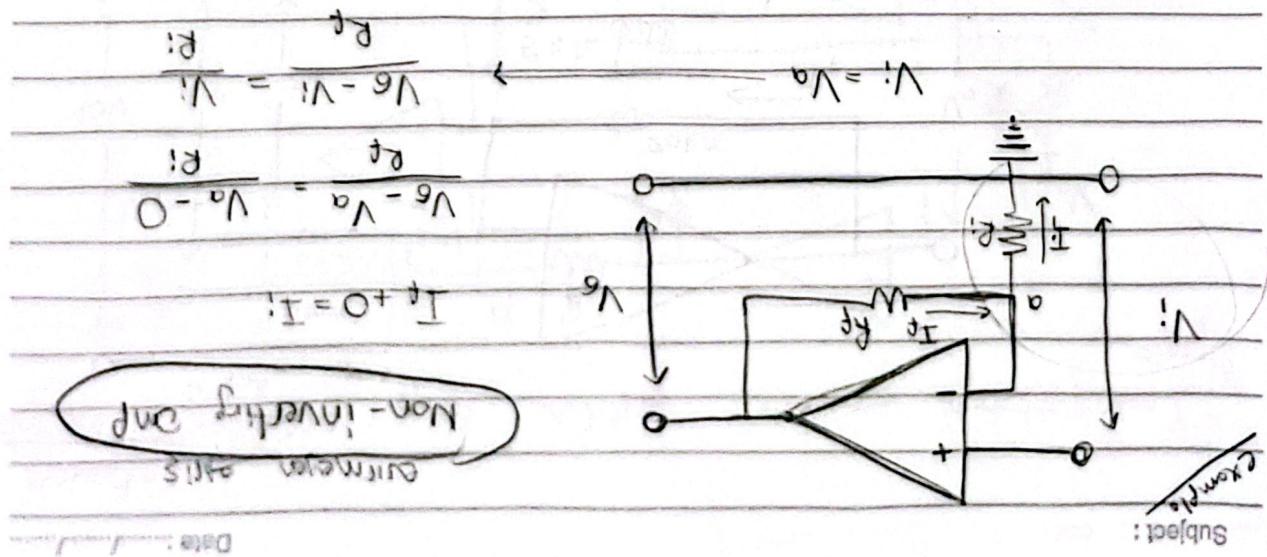
$$V_0 = V_1 \cdot \left(1 + \frac{R_f}{R_1}\right)$$



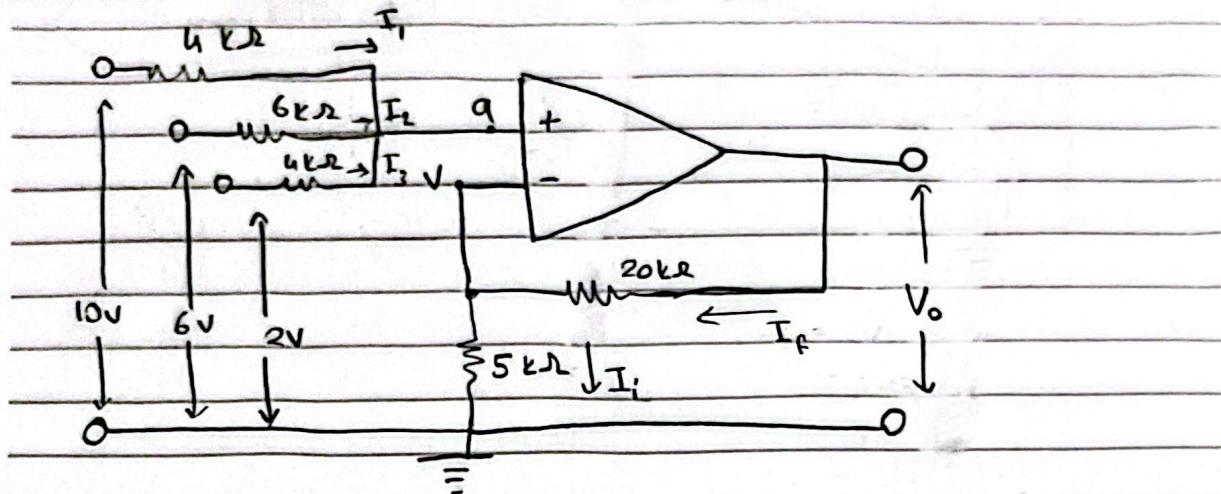Example:

$$V_o = R_f \left(\frac{V_1 + V_2 + V_3}{R_1} \right) \left(1 + \frac{R_f}{R_i} \right)$$


$$\frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$V_o = \frac{3}{2} \left(\frac{10}{6} + \frac{6}{6} + \frac{2}{6} \right) \left(1 + \frac{20}{5} \right)$$

$$\frac{3}{2} = \frac{1}{R_i}$$

$$V_o = \frac{3}{2} \cdot \frac{96}{24} \cdot \frac{25}{5} = 20.3 = 30 \text{ V} = V_o$$

$$\text{Gain} = \left(1 + \frac{R_f}{R_i} \right) = 5 = \text{Kontang}$$

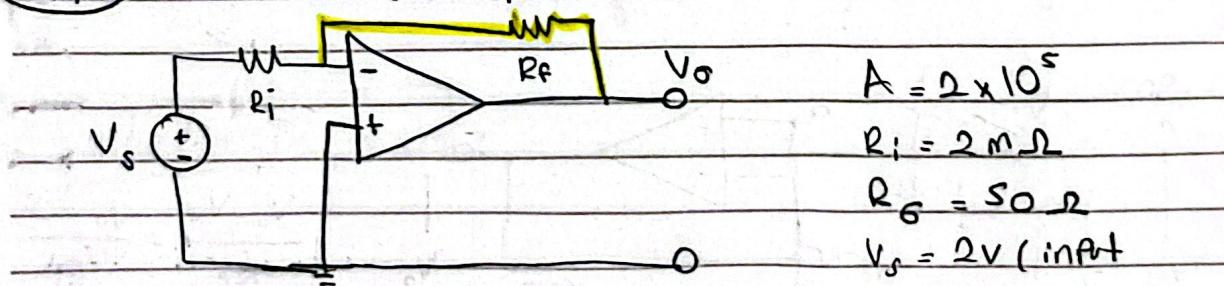Example - open loop vs closed loop -

$$\text{Open loop gain} = ? \quad V_o = A V_s = 2 \times 10^5 \cdot 2V = 400,000 \text{ V}$$


$V_o = V_{oc}$ Saturated

Closed loop gain = ?

$$(R_f = 20k\Omega) \quad V_o = -\frac{R_f}{R_i} \cdot V_s = -\frac{20}{10} \cdot 2V = -4V$$


Instrumentation amplifier

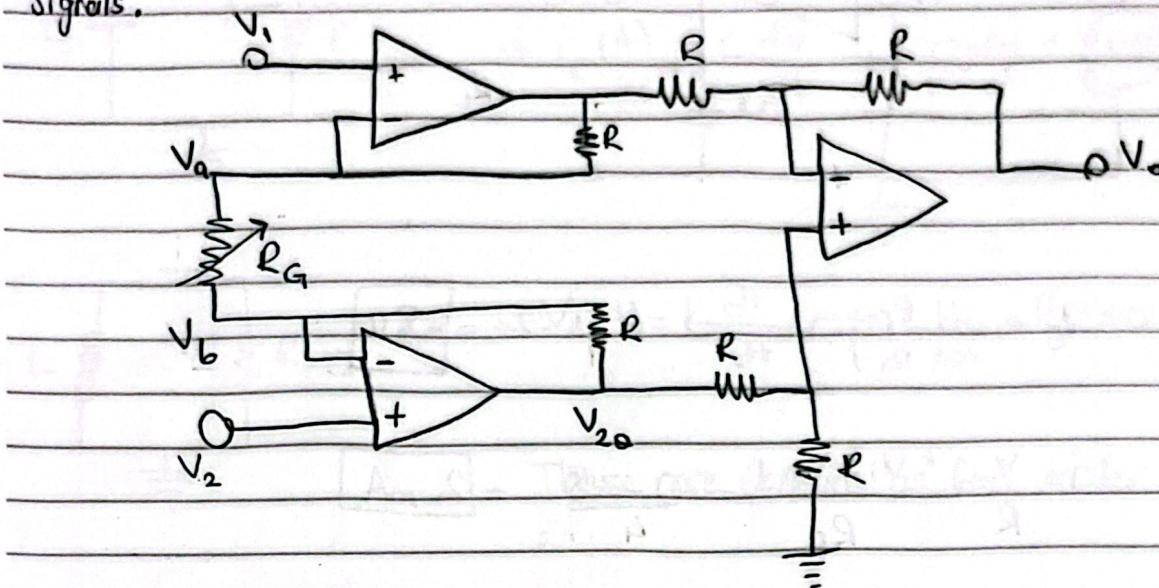amplifies small differences in the input signals.




$$V_{\text{out}} = \underbrace{\left(1 + \frac{2R}{R_G}\right)}_{\text{gain}} (V_2 - V_1)$$

Summary

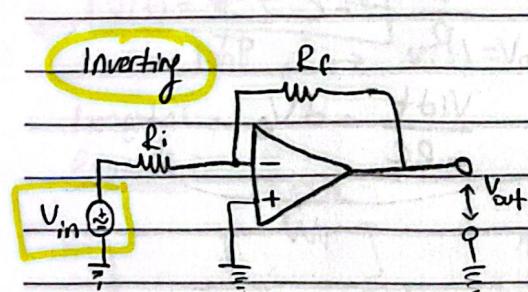

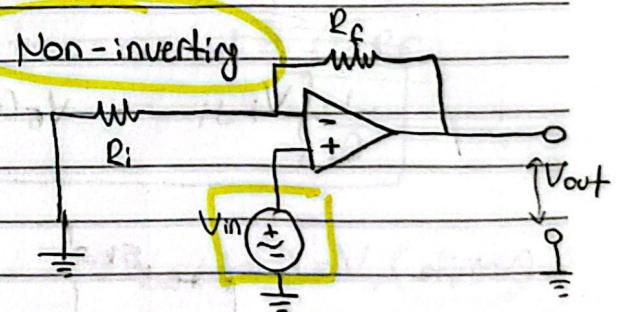
$$V_{\text{out}} = -\frac{R_f}{R_i} V_{\text{in}}$$



$$V_{\text{out}} = \left(1 + \frac{R_f}{R_i}\right) V_{\text{in}}$$

Voltage follower (Gain amplifier)

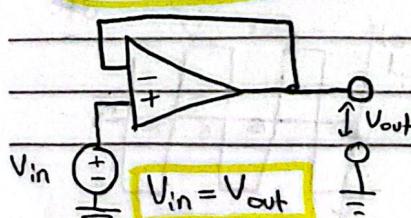


$$V_{\text{in}} = V_{\text{out}}$$


Summing amplifier

$$\rightarrow V_{\text{out}} = -\frac{R_f}{R_i} (V_1 + V_2 + \dots)$$

Difference amplifier


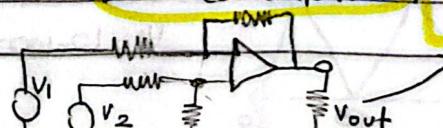
$$\rightarrow V_{\text{out}} = V_2 - V_1$$




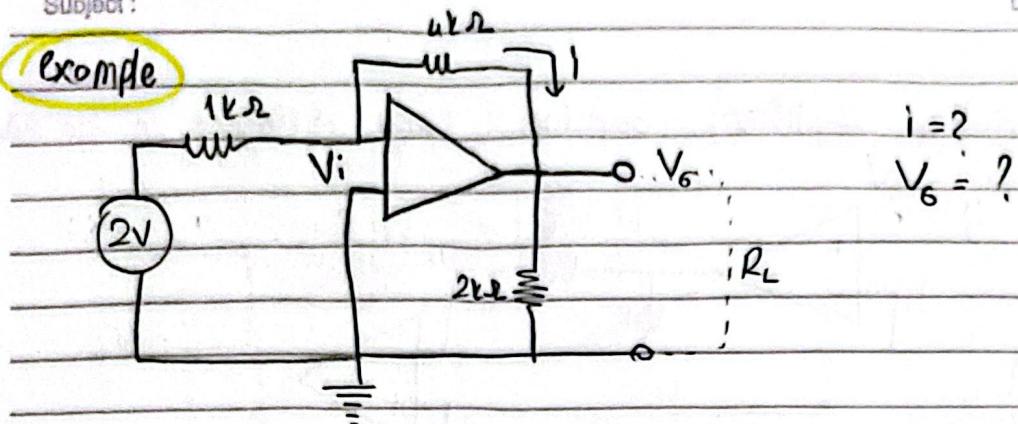
Example

$$V_6 = -\left(\frac{R_F}{R_i}\right) \cdot V_{in} \rightarrow -\frac{4}{1} \cdot 2 = \boxed{-8V}$$

$$i = \frac{V}{R} = \frac{V_i - V_6}{R_F} = \frac{0 - -8}{4} = \boxed{2 \text{ mA}}$$

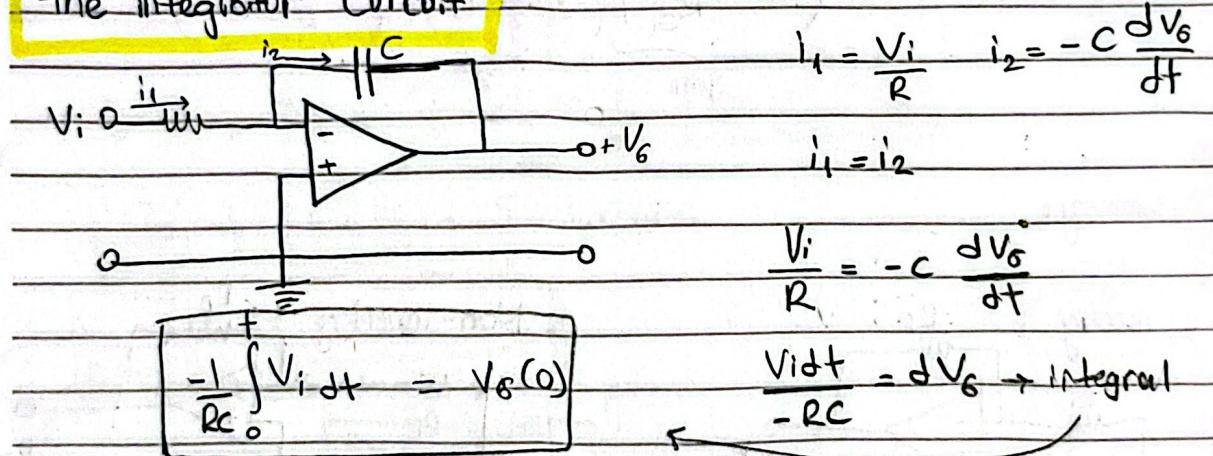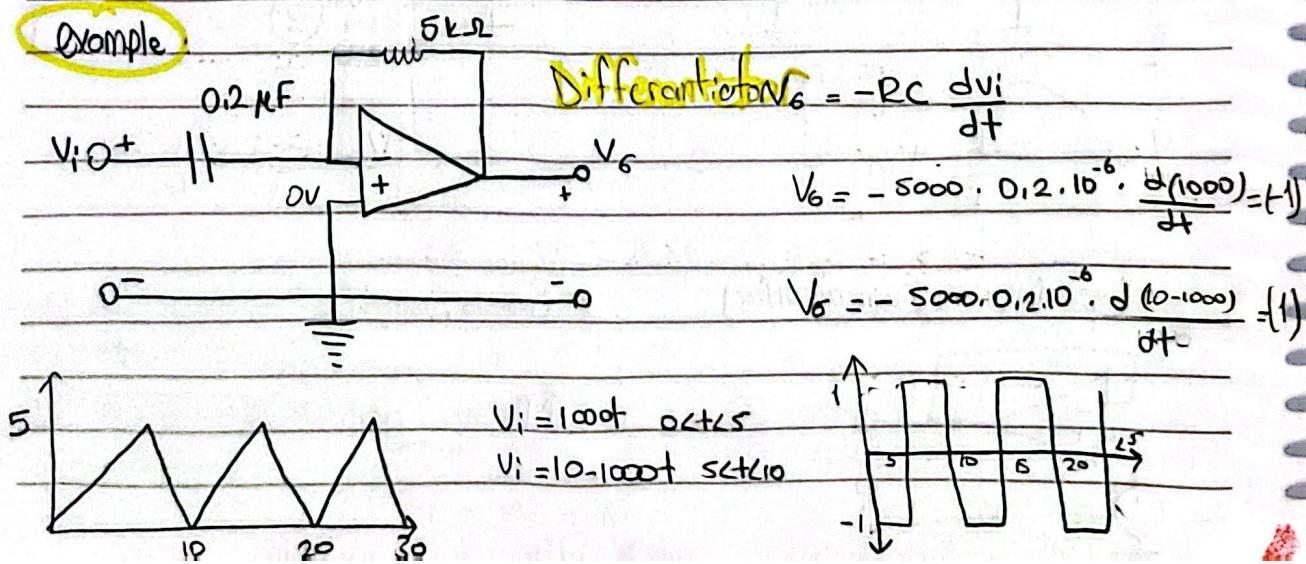the integrator Circuit**Example**

RC and RL Circuits

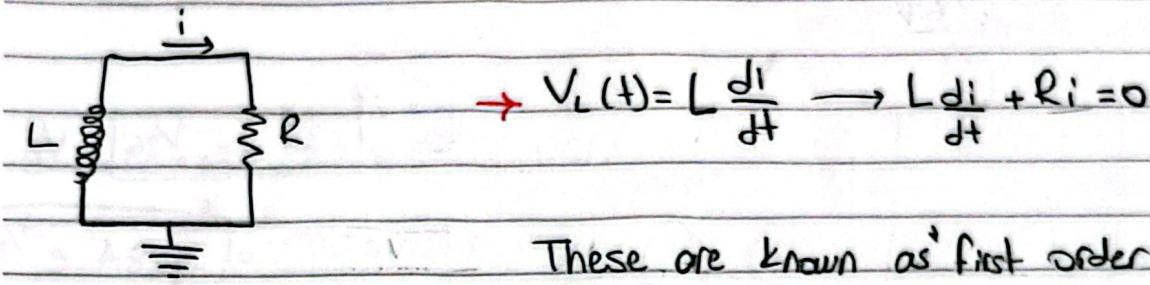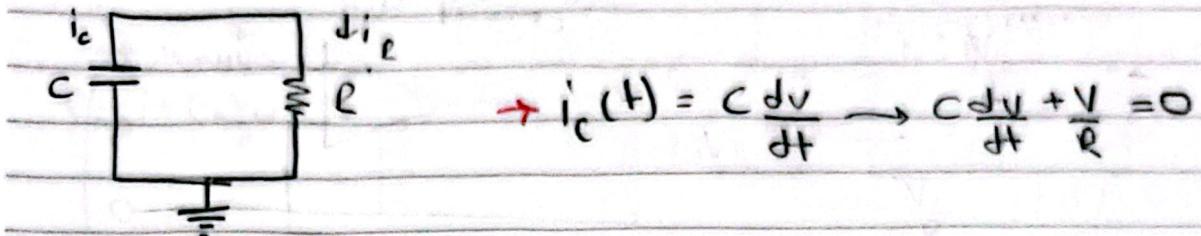

These are known as "first order circuits"


RC circuit

$$i_c + i_e = 0$$

$$C \frac{dv}{dt} = \frac{V}{R}$$


$$V(t) = V_0 e^{-t/\tau_{RC}}$$

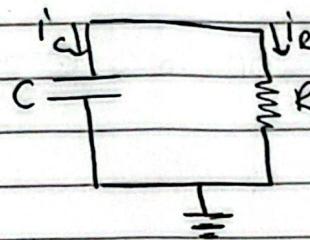when time $t \rightarrow 0$ $\rightarrow V(t) = V_0$



$$\text{time constant} = \boxed{\tau = RC}$$

Example :

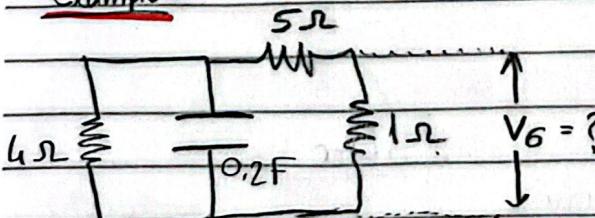


$$V_C(t=0) = V_0$$

$$\tau = RC = 2.4 \cdot 0.2 = 0.48$$

$$R_{eq} = \frac{4 \cdot 6}{4+6} = \frac{1}{4} + \frac{1}{6} = 2.4 \Omega$$

$$V_C(t) = V_0 e^{-t/\tau} = \frac{1}{T+5} \cdot e^{-t/0.48} = \boxed{\frac{1}{6} e^{-t/0.48}}$$

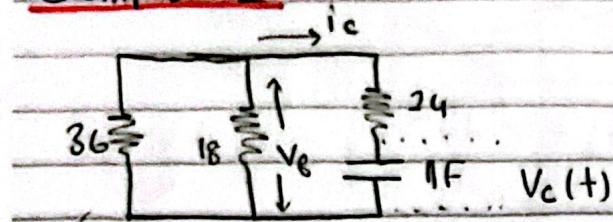example - 2 - :

$$V_C(t=0) = 10V$$

$$V_C = ? \quad V_B = ? \quad i_C = ?$$


$$\frac{36 \cdot 18}{36+18} = \frac{1}{36} + \frac{1}{18} = \frac{3}{36} = \frac{1}{12}$$

$$\frac{12}{12+24} \cdot 10V \cdot e^{-t/36} = 3.33V e^{-t/36} = V_B$$

$$i_C = \frac{V_B}{R_B} = \frac{3.33V e^{-t/36}}{12} = 0.28A \cdot e^{-t/36}$$

$$36 \cdot 1 = 36 \text{ sec} = \tau \rightarrow V_C(t) = 10V \cdot e^{-t/36} = V_C$$

$$\text{or } i_C = C \frac{dV}{dt}$$

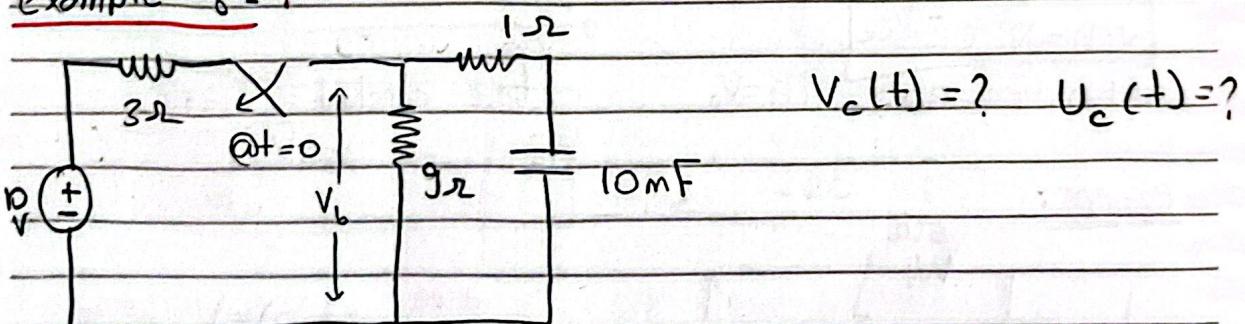example - 3 - :

$$V_C(t) = ? \quad U_C(t) = ?$$

before:

$$V_B = \frac{9}{9+3} \cdot 10V$$

$$V_B = 7.5V = V_{OC}$$

$$U = \frac{1}{2} C V_0^2 = \frac{1}{2} \cdot 10 \cdot (7.5)^2 = 0.28J$$

after:

$$V_C(t) = V_0 e^{-t/\tau}$$


$$\tau = 10 \cdot 0.001 = 0.01$$

$$V_C(t) = 7.5 \cdot e^{-t/0.01}$$

$$U_C(t) = \frac{1}{2} C [V_C(t)]^2$$

Subject :

Date :

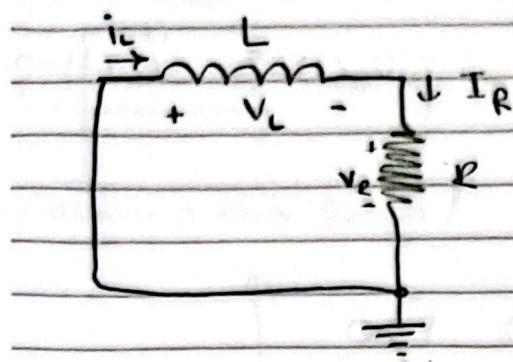RL circuit:

$$V_L = L \frac{di}{dt} \quad U(t=0) = \frac{L}{2} L I^2$$

KVL:

$$V_L + V_R = 0$$

$$i(t=0) = I_0 = B C^0$$

$$I_0 = B$$



So

$$L \frac{di}{dt} + i_R R = 0$$



$$\tau = \frac{L}{R}$$

$$i(t) = B e^{-t/\tau}$$

$$\boxed{i(t) = I_0 e^{-t/\tau}}$$

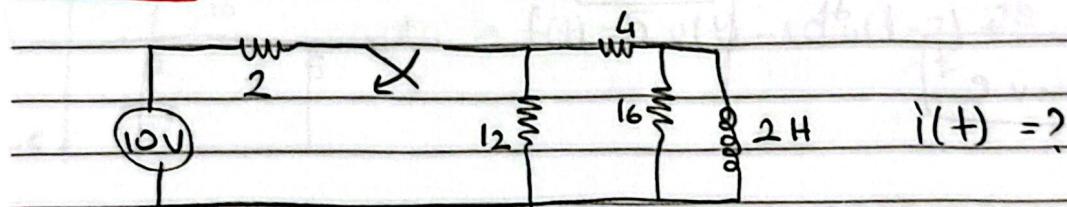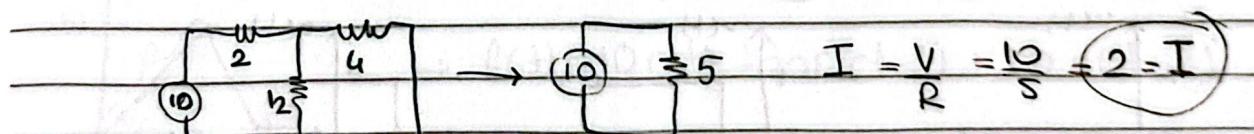example :★ when $t < 0$ (the inductor \rightarrow short circuit)


$$I_0 = I\left(\frac{12}{4+12}\right) = 2A \cdot \frac{12}{16} = \boxed{1.5 A}$$

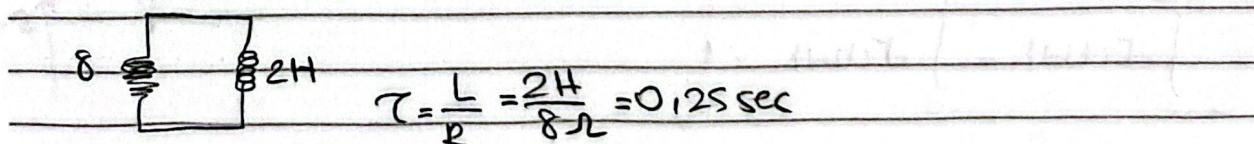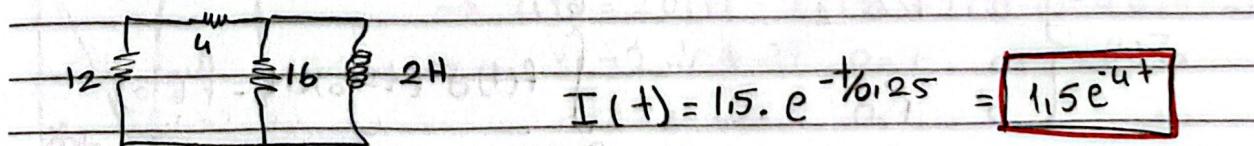★ when $t > 0$ 

$$\frac{2+3}{2} = \frac{5}{2}$$

$$\frac{B+2}{2}$$

Subject:

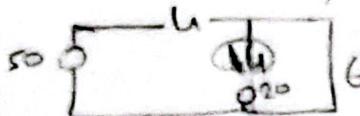


$$\frac{10 - 6}{10 + 6} = \frac{4}{16} = \frac{1}{4}$$


$$-70 \quad 8.2 =$$

Date: _____

Example - 2-

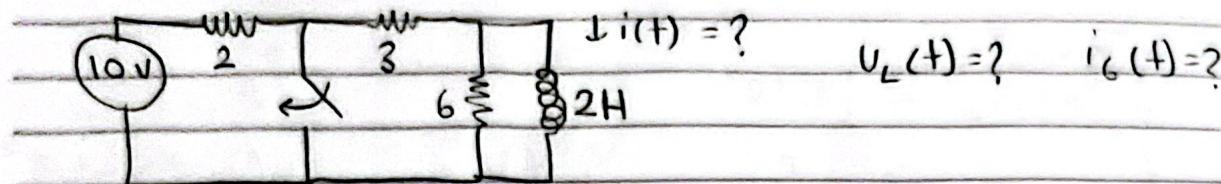


* + < 0

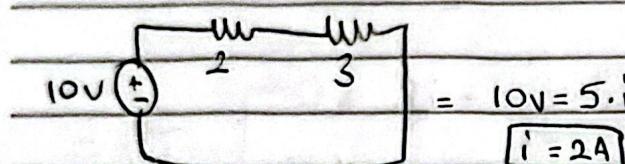

$$i_L(t) = -\frac{L}{R} v e^{-t} = -\frac{3}{4} A e^{-t}$$

* + > 0

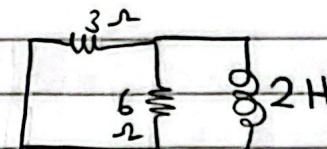


$$\tau = \frac{L}{R} = \frac{2H}{2\Omega} = 1 \text{ sec}$$

$$V_L = L \frac{di}{dt} = 2H \cdot \frac{d(2e^{-t})}{dt} \quad | \quad 2 \cdot e^{-t} \leftarrow i(t) = i_L(t=0) \cdot e^{-t}$$

$$V_L = -L v e^{-t}$$

the unit step Functions

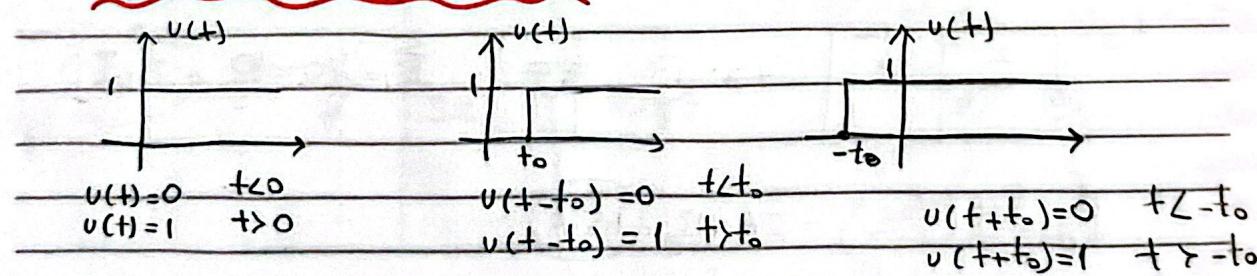

* Delta function δ(t)

$$\delta(t) \begin{cases} 0 & t < 0 \\ \infty & t = 0 \\ 0 & t > 0 \end{cases}$$

$$\int_a^b f(t) \delta(t-t_0) dt = f(t_0)$$



$$\int_{-\infty}^{+\infty} \delta(t) dt = \int_{-0}^{+0} \delta(t) dt = 1$$




Subject :

Date : _____


the Ramp function :

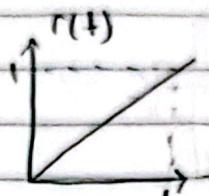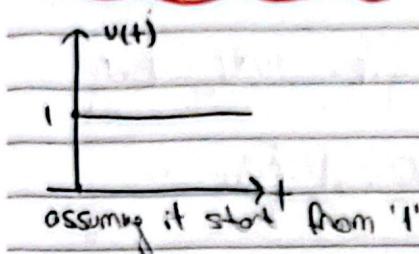
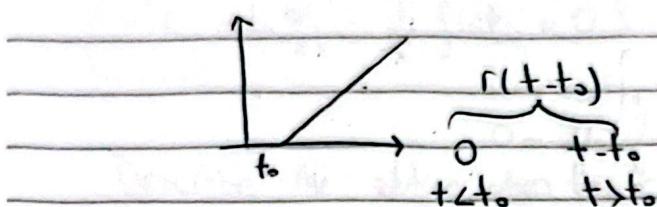
$$r(t) = \int_{-\infty}^t u(\tau) d\tau = t u(t)$$





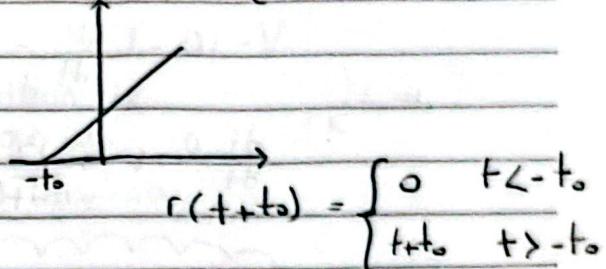
$$r(t) = \begin{cases} 0 & t < 0 \\ t & t > 0 \end{cases}$$




$$r(t+t_0) = \begin{cases} 0 & t < -t_0 \\ t+t_0 & t > -t_0 \end{cases}$$

examples

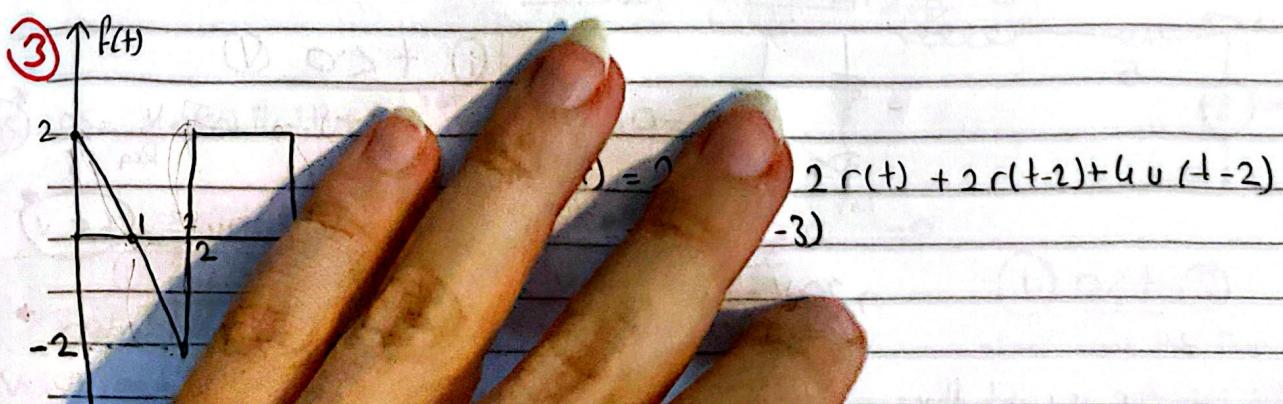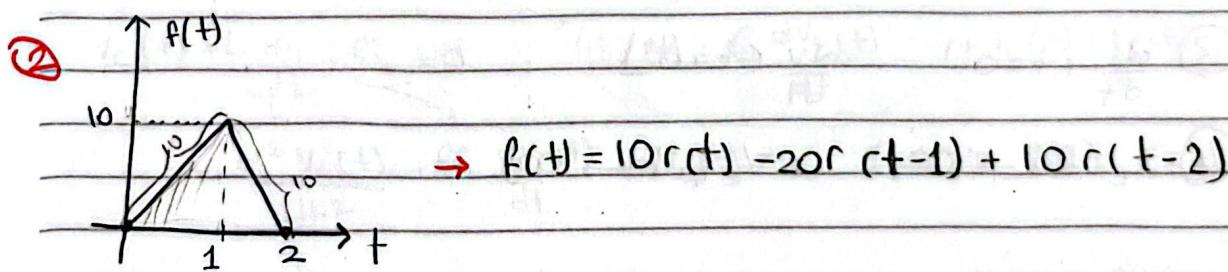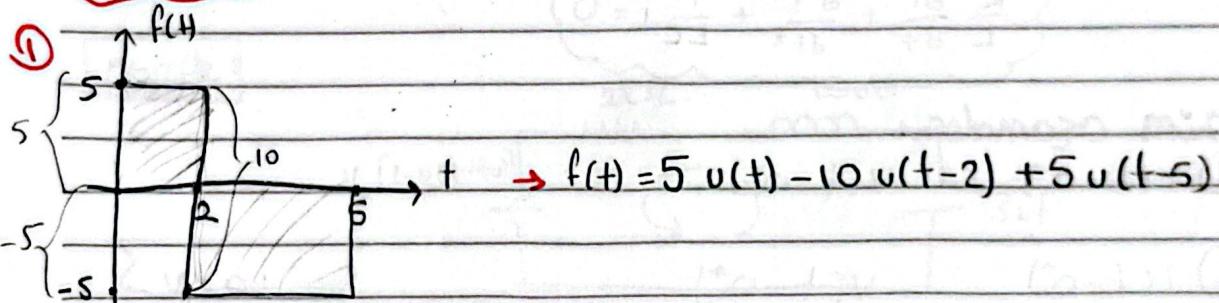

Second Order Circuit :

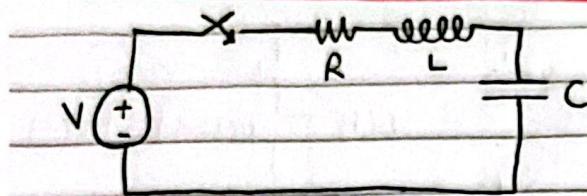

$$V_R = iR \quad V_L = L \frac{di}{dt}$$

$$V_C = \frac{1}{C} \int i dt$$

KVL :

$$V - iR - L \frac{di}{dt} - \frac{1}{C} \int i dt = 0$$

derivative

$$\frac{di}{dt} R + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

divide by L

$$\frac{R}{L} \frac{di}{dt} + \frac{d^2i}{dt^2} + \frac{1}{LC} i = 0$$


Gözüm oğamaları :

$$\textcircled{1} \quad i(t=0^-) \quad V(t=0^-)$$

$$\textcircled{2} \quad i(t=0^+) \quad V(t=0^+)$$

$$\textcircled{3} \quad \frac{di}{dt}(t=0^+) \quad \frac{dv}{dt}(t=0^+)$$

$$\textcircled{4} \quad i_L(t \rightarrow \infty) \quad V_C(t \rightarrow \infty)$$

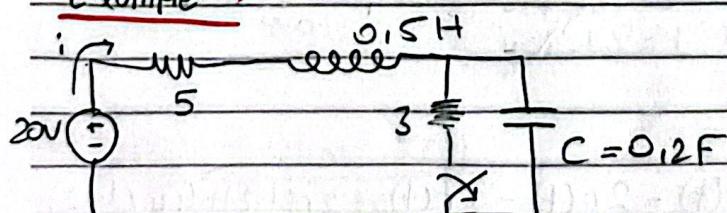Example :

$$\textcircled{1} \quad + < 0 \quad \checkmark$$

$$i(0^-) = i(0^-) = \frac{V}{R_{eq}} = \frac{20}{8} = 2.5$$

$$V_C(0^-) = 20V \cdot \frac{3}{8} = 7.5V$$

$$\textcircled{2} \quad + > 0 \quad \checkmark$$

will still same cause

$$20V - (2.5)(5) - V_L - 7.5V = 0 \quad \textcircled{4} \quad t \rightarrow \infty \quad \checkmark$$

$$V_L = 0$$

$$i_L(t \rightarrow \infty) = 0$$

$$V_C(t \rightarrow \infty) = 20V$$

the inductor is right there

$$i(0^+) = 2.5 \quad V(0^+) = 7.5$$

$$\textcircled{3} \quad i_L / r = \frac{dv_L}{dt} = \frac{2.5}{1} = 2.5V \quad \frac{di}{dt} = \frac{V_L}{1} = 2.5A \quad \text{to find } V_L \rightarrow \frac{di}{dt} = \frac{V_L}{1} = 2.5A$$


Subject :

Date _____

Source free RCL circuit

Using KVL :

$$-V_R - V_L - V_C = 0$$

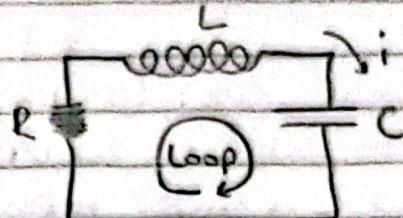

$$-iR - L \frac{di}{dt} - \frac{1}{C} \int i dt = 0$$


Describe the solution when the condition is

1- Overdamped $\rightarrow \alpha > \omega_0$

2- Critically damped $\rightarrow \omega_0 = \alpha$

3- underdamped $\rightarrow \omega_0 > \alpha$

Example:

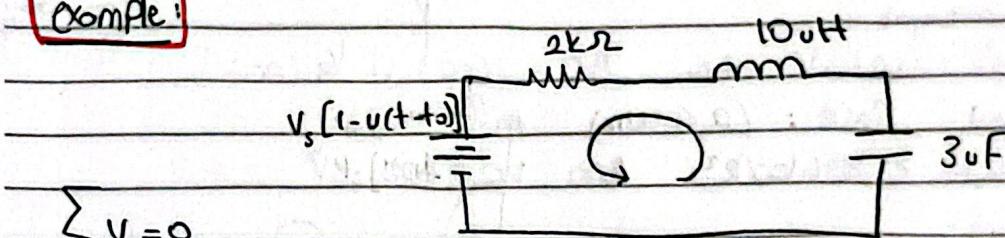

$$V_C(t) + L \frac{di_L}{dt} + R i_L = 0 \quad i_C(t) = C \frac{dV_C(t)}{dt} \quad i_L(t) = i_C(t)$$

$$LC \frac{d^2 V_C(t)}{dt^2} + RC \frac{dV_C(t)}{dt} + V_C(t) = 0 \quad (LC \text{ ye böl})$$

$$\frac{d^2 V_C(t)}{dt^2} + \frac{R}{L} \frac{dV_C(t)}{dt} + \frac{V_C(t)}{LC} = 0$$

$$\text{Let } V_C(t) = A e^{st}$$

$$As^2 e^{st} + \frac{AR}{L} s e^{st} + \frac{A}{LC} e^{st} = 0$$

$$a = R/2L$$

$$Ae^{st} \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = 0$$

$$w = \frac{1}{\sqrt{LC}}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Delta = b - \sqrt{4ac}$$

$$s^2 + 2as + w^2 = 0$$

$$s_1, s_2 = \frac{-b \pm \sqrt{\Delta}}{2a}$$

* three types of Solutions :


1- Overdamped Case : ($\alpha > \omega_0$)

implies that $C > 4L/R^2$

S_1 and $S_2 \rightarrow$ negative + real

$$\rightarrow V_C(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

en hizli inan

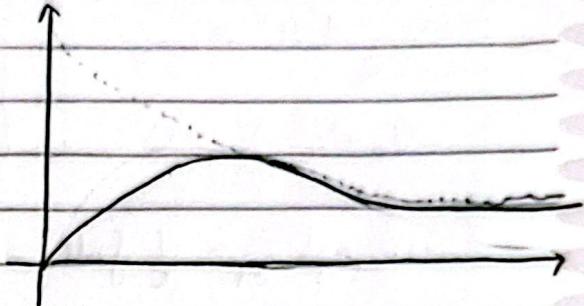


2- Critically damped Case : ($\alpha = \omega_0$)

implies that $C = 4L/R^2$

$$S_1 = S_2 = -\alpha = -R/2L$$

$$\rightarrow V_C(t) = A_1 e^{-\alpha t} + A_2 \Delta t e^{-\alpha t}$$

en erken yakinsayon

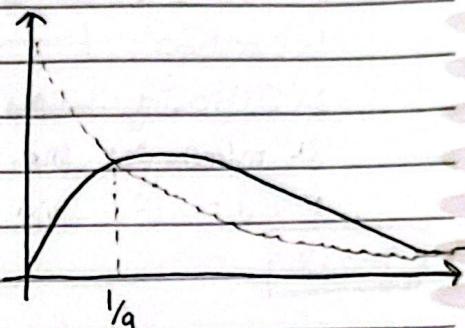

3- Underdamped Case : ($\alpha < \omega_0$)

implies that $C < 4L/R^2$


- en çok salınım -

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha + j\omega_d$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha - j\omega_d$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$j = \sqrt{-1} \rightarrow (i)$$

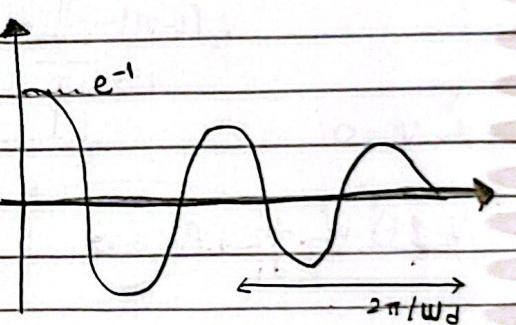

$$V_C(t) = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) \rightarrow \text{for } (\omega_d t = \theta)$$


$$V_C(t) = e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$

(*) Sadece Paralel veya Seri oldugu zaman a degisir

$$\text{Parallel} \rightarrow a = \frac{1}{2RC}$$

$$\text{Series} \rightarrow a = \frac{R}{2L}$$

Series RLC Network (with Source)

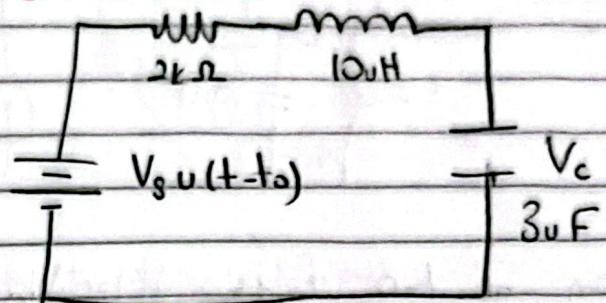

$i(t_0) = i_L(t_0) = 0A$ and $V_c(t_0) = 0V$ - initially -

$$V_L(t_0) = 0V \quad i_c(t_0) = 0A$$

→ when V_s at $t \geq t_0$, Replace the capacitor with open circuit and the inductor with a short circuit.

$$i(\infty) = i_L(\infty) = 0A \quad \text{and} \quad V_c(\infty) = V_s$$

$$V_L(\infty) = 0V \quad \text{and} \quad i_c(\infty) = 0A$$


$$\frac{d^2 V_c(t)}{dt^2} + \frac{R}{L} \frac{dV_c(t)}{dt} + \frac{1}{LC} V_c(t) = \boxed{V_s} / LC$$

for L

* help Sabit dan formoller *

$$- i_c(t) = C \frac{dV_c(t)}{dt} \quad - i(t) = i_c(t) = i_L(t) = i_R(t)$$


$$- V_L(t) = L \frac{di_L(t)}{dt} \quad - V_R(t) = R i_R(t)$$

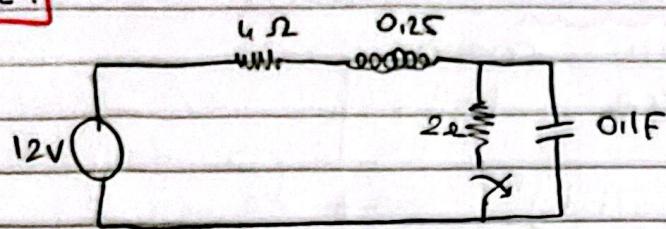Example :


the switch open at $t=0$. finds $i(t=0^+)$, $v(t=0^+) = ?$

$$\frac{di(t=0)}{dt}, \frac{dv(t=0^+)}{dt} = ?$$



Steady state \rightarrow inductor = short
capacitor = open

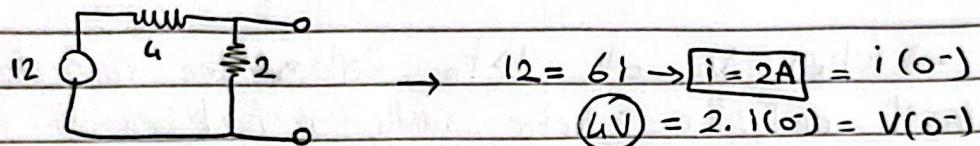 $(t=0^-)$  $(t=0^+)$
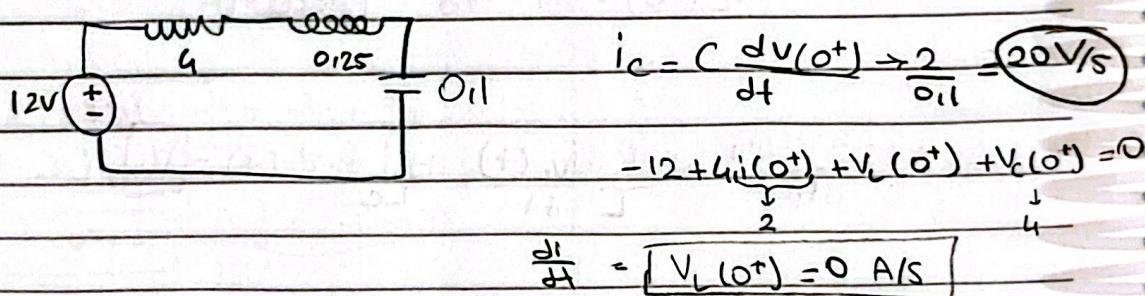
$$i(0^+) = i(0^-) = 2A \quad v(0^+) = v(0^-) = 4V$$




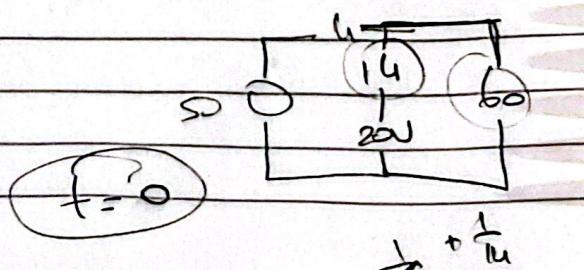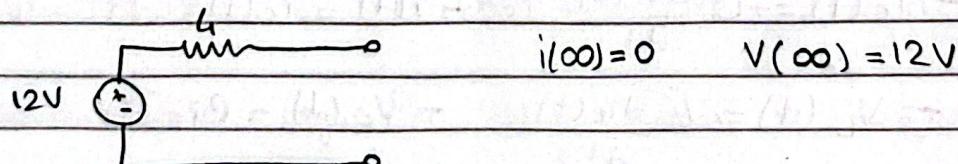$(t=\infty)$ steady state $\rightarrow L \rightarrow$ short, $C \rightarrow$ open



$$\begin{aligned}
 & \text{Circuit Diagram:} \\
 & \text{Left branch: } \frac{1}{R+L} = \frac{1}{15} \quad \text{Right branch: } \frac{1}{R+L} = \frac{1}{15} \\
 & \text{Bottom loop: } 30 - 8 - 10 - 3R = 0 \quad \text{Top loop: } 3R + 20 = 60 \\
 & \text{Node analysis: } V_0 = 12 - \frac{1}{2}V_L \quad V_L = 12 - 2V_0 \\
 & \text{Voltage drop across } R: V_R = 12 - 2V_0 \\
 & \text{Current through } R: I_R = \frac{V_R}{R} = \frac{12 - 2V_0}{15} \\
 & \text{Current through } L: I_L = \frac{dV_L}{dt} = \frac{1}{2}V_R = \frac{1}{2}(12 - 2V_0) = 6 - V_0 \\
 & \text{Total current: } I = I_R + I_L = \frac{12 - 2V_0}{15} + 6 - V_0 = \frac{12 - 2V_0 + 90 - 15V_0}{15} = \frac{102 - 17V_0}{15} \\
 & \text{Substituting into top loop: } 30 - \frac{102 - 17V_0}{15} - 10 - 3R = 0 \\
 & \text{Simplifying: } 30 - \frac{102 - 17V_0}{15} - 10 - 3(15) = 0 \\
 & \text{Solving for } V_0: 30 - \frac{102 - 17V_0}{15} - 10 - 45 = 0 \\
 & 30 - \frac{102 - 17V_0}{15} - 55 = 0 \\
 & \frac{102 - 17V_0}{15} = 25 \\
 & 102 - 17V_0 = 375 \\
 & 17V_0 = 273 \\
 & V_0 = 16.05 \text{ V}
 \end{aligned}$$
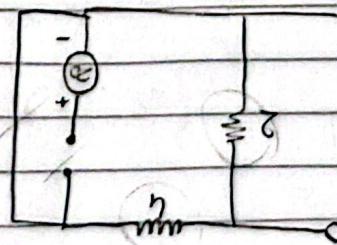
$$I_{(O^-)} = V_R(O^-) = 0 \quad V_C(O^-) = -20 \text{ V}$$



$$V_R(\infty) = 0$$

$$i = i(\infty) e^{-\frac{t}{RC}} = i(\infty) e^{-\frac{t}{0.6H}}$$


$$i = i(\infty) \frac{e^{\frac{t}{0.6H}}}{e^{\frac{t}{0.6H}} + 1}$$

Steady state $\rightarrow t \rightarrow \infty$

$$i(\infty) = 0$$

$$i = \frac{1}{R} V_R(O^-) = \frac{1}{15} \cdot 20 = \frac{4}{3} \text{ A}$$

$$V_C(O^-) = ?$$

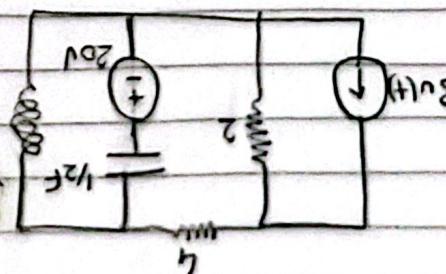

Example:

Date _____

Subject _____